


Decoherence

* Understand basic operation, see imperfect data,
go deeper into importance issue of qu. coherence
(gate errors).

This is main issue facing qubits.

* Go into some detail how

* What to worry about

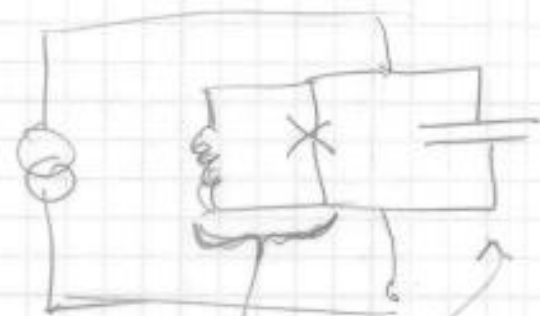

① S.C. + Josephs. effect
(where does non-linearity come from?)

② Leads; dissip from circuit
(+ ext'l noise).
- Microwave Engineering -

③ Capacitor (2-level states)

↳ $1/f$ noise Φ, Φ_0

Circuit Engineering + Decoherence

Gate errors need to be calculated!



bath (other qubit modes)

↳ coupling to bath, entangles qubits with other modes.

But since don't meas. bath, lose info about quantum state.

Nice general model - but how calculate anything?

(1) Need to model decoh. (bath) - Do this with circuit elements, particularly R's.

* No one bath, because it depends on how you build the circuit! (unlike atoms + vacuum)
(+ this interest in field!)

* Either measure or model circuit and R's, so need general theory of decoherence.
(what really matters in design!)

(2) Show Decoherence = Noise + Dissipation
(Diss = $Q \times \text{Noise}$)

Very general + powerful model!
"See" how to design qubits

But, will have to learn

- Circuit theory
 - Microwave Eng.
 - Noise
- (classical)
(+ q)

Then Connection to Q.M.

Circuits

① Basic circuit elements, linear response $Z \circ$

$$\frac{V}{I} = R$$



$$\frac{V}{I} = Z = i\omega L$$

$(v = L \frac{dI}{dt})$



$$Z = \frac{1}{i\omega C}$$



$(v = \frac{Q}{C})$




② Response of multi-elements



$$=$$

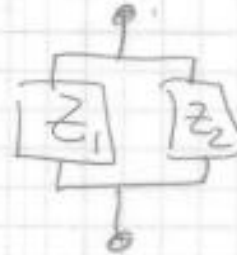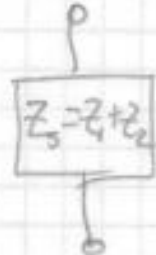

$$=$$

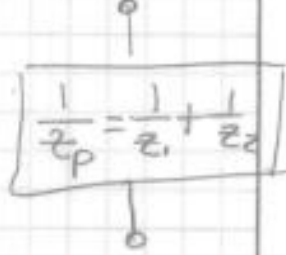

③ Sources:

voltage



$$R_{dyn} = 0$$

current



$$R_{dyn} = \infty$$

Flux



$$= \int v dt$$

charge




$$Q = \int I dt$$

④ Thevenin Equiv's:




$$= \frac{V}{R}$$

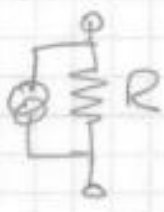

$$\Rightarrow$$




$$= \frac{Q}{C}$$

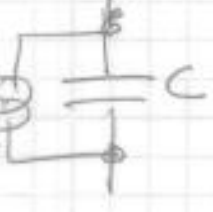


$$\Downarrow$$


$$\Rightarrow$$

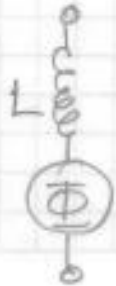

$$= \frac{\Phi}{L}$$

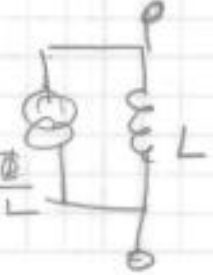

Resonator (Simple model of qubit)

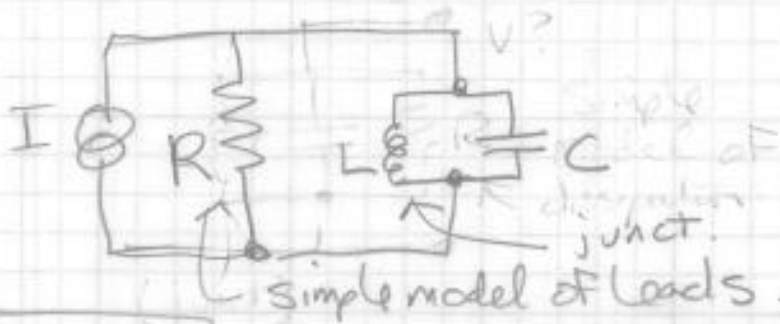

Freq. Domain
(spectroscopy)

$$\frac{1}{Z} = \frac{1}{i\omega L} + i\omega C + \frac{1}{R}$$


respon $\frac{V}{I} = Z_x =$

$$\frac{1}{\frac{1}{i\omega L} + i\omega C + \frac{1}{R}}$$

Freq. dependent,
complex (ϕ shift -
Input I to out V)

$$\omega = \omega_0 + \Delta\omega$$

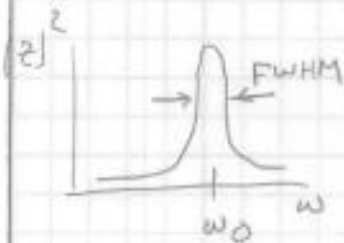max when $= 0$ $\frac{1}{\omega L} = \omega C$
reson. freq. $\Rightarrow \omega_0^2 = \frac{1}{LC}$



$$\approx \frac{1}{\frac{1}{L^2 C^2} \left(1 - \frac{\Delta\omega}{\omega_0}\right)^2 + i(\omega_0 + \Delta\omega)C + \frac{1}{R}}$$

$$= \frac{1}{2i\Delta\omega C + \frac{1}{R}}$$

$$|Z|^2 \propto \frac{1}{(2\Delta\omega C)^2 + \left(\frac{1}{R}\right)^2} \propto \frac{1}{(\Delta\omega)^2 + \left(\frac{1}{2RC}\right)^2}$$


$$FWHM = 2 \frac{1}{2RC} = \frac{1}{RC}$$

HM $\Rightarrow \Delta\omega = \frac{1}{2RC}$

$$Q \equiv \frac{\omega_0}{FWHM} = \frac{\omega_0 RC}{\frac{1}{2RC}} = \frac{R}{\omega_0 C}$$

\leftarrow Ratio $\frac{\omega_0}{\Delta\omega}$
 \leftarrow Dissip
 $\leftarrow Z$ resonator

Time Domain

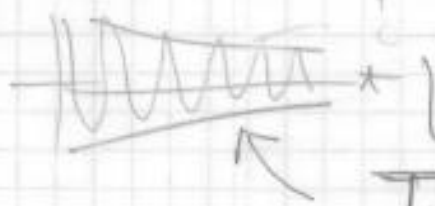

$$T_{1/e} = RC$$

So $Q \sim$ # oscillations

before lose energy

Energy Decay (T_1) of qubits

- This easy to understand from classical analysis (what know already!)

1) Imagine H.O. (resonator) weakly excited
 (spectroscopy or pulsed excitation)
 $|1\rangle$ state small ampl.
 ($|2\rangle$ state negligible)

2) Then only $1 \rightarrow 0$ transitions matter,
 just like a qubit

$$T_1 = RC \left| \frac{\langle 0 | \hat{\delta} | 1 \rangle_{\text{qubit}}}{\langle 0 | \hat{\delta} | 1 \rangle_{\text{H.O.}}} \right|^2$$

3)

Since H.O., $Q = \text{class.}$

\uparrow Cor. Fact. ≈ 1 mostly,
 (At least good approx.)

Qubit with correction


Since slightly
non-linear

4) Proper calculations give this result.

5) Power of this calculation -
 Can do general model very easily

More General Model

M (beyond dissip. = R)

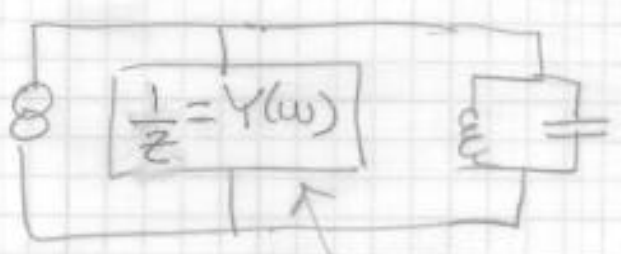

Arbitrary admittance of leads.



$$\frac{1}{Z_x} = \frac{1}{\frac{1}{i\omega L} + i\omega C + i \operatorname{Im} Y(\omega) + \operatorname{Re} Y(\omega)}$$

= 0 @ reson.

(Dissipative part
Dispersive part)

Assuming effect of Y is small (pert. thx around ω_0)

$$2i\delta\omega C + i \operatorname{Im} Y(\omega_0) = 0$$

(unperturbed resonance)

shift in Res Freq.

$$\delta\omega = \frac{\operatorname{Im} Y(\omega_0)}{2C} \quad (+ \text{small Lamb shift when do Q.M.})$$

$$\frac{1}{R} = \operatorname{Re} Y(\omega_0)$$

$$\left(T_1 = \frac{C}{\operatorname{Re} Y(\omega_0)} \right)$$

$Y(\omega_0)$ matters
↑ only near/at resonance for T_1

Transmission Lines


(Like discussing simple lumped circuits)

Lumped Circuit; size $\ll \lambda$ (wavelength)

At μ waves, $\lambda \sim 1\text{cm}$; size effects?

t-lines show behavior (quant. + qual.)

(+ how to model a Resistor in Q.M.)

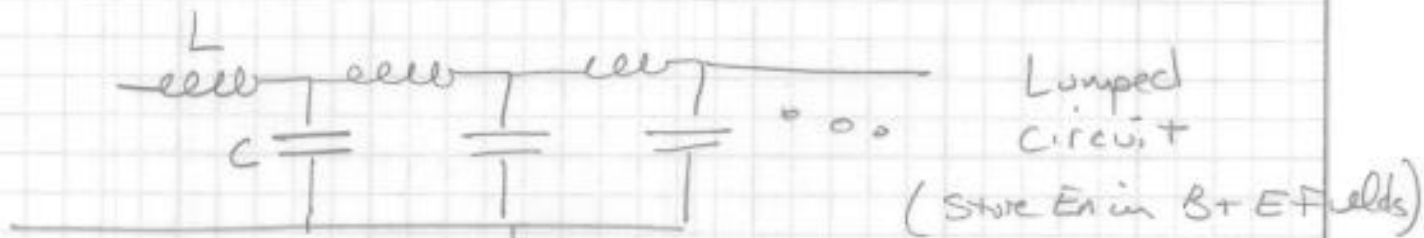

$$L = \mu_0 \mu_r \frac{1}{c^2} \frac{d}{l} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \begin{array}{l} \text{induct + Cap per} \\ \text{unit length} \end{array}$$

$$C = \frac{q_c \epsilon_r \epsilon_0 l}{c^2} \quad \left(\begin{array}{l} \mu \approx \mu_0 \\ \epsilon = \epsilon_r \epsilon_0 \text{ (}\epsilon_r \sim 10 \text{ often)} \end{array} \right)$$



$$Z_0 = Z_L + \frac{1}{\frac{1}{Z_C} + \frac{1}{Z_0}}$$

$$(Z_0 - Z_L) = \frac{Z_C Z_0}{Z_C + Z_0}$$

$$(Z_0 - Z_L)(Z_0 + Z_L) = Z_0 Z_C$$

$$Z_0^2 + Z_0 Z_L - Z_L Z_C - Z_L Z_0 = Z_C Z_0$$

$$Z_0^2 = Z_C Z_0$$

$$Z_0 = \pm \sqrt{Z_L Z_C} \equiv \pm Z_0$$

$$Z_0 = \sqrt{\frac{j\omega L}{j\omega C}}$$

$$= \sqrt{\frac{g_L \mu l}{g_C \epsilon l}}$$


$$= \sqrt{\frac{\mu_0}{\epsilon_0}} \sqrt{\frac{g_L \mu_r}{g_C \epsilon_r}}$$

$$= 377 \Omega \cdot \sqrt{\quad} \quad \text{Typical geometries}$$

$$\approx 50 \Omega$$

① Transmission Line "Looks" like a 50Ω resistor

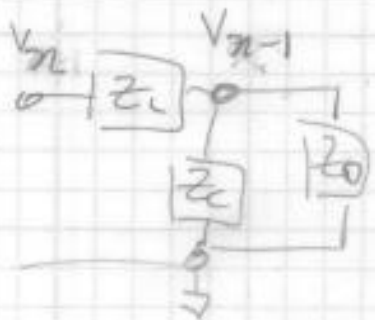Why? No dissipation Very strange!
 → Signal propagates down line, never reflecting since so long!



Voltage divider

$$V_C = I \cdot Z_C$$

$$V_C = \frac{V}{Z_0 + Z_C} \cdot Z_C$$

$$\frac{V'}{V} = \frac{Z_C}{Z_0 + Z_C}$$

$$\frac{V_{n-1}}{V_n} = \frac{V_C}{V_{n-1}} = \frac{(Z_0 \parallel Z_C)}{Z_L + (Z_0 \parallel Z_C)}$$

$$= \frac{1}{1 + Z_L \left(\frac{1}{Z_0 \parallel Z_C} \right)}$$

$$= \frac{1}{1 + Z_L \left(\frac{1}{Z_0} + \frac{1}{Z_C} \right)}$$

$$= \frac{1}{1 + \frac{Z_L}{\sqrt{Z_0 Z_C}} + \frac{Z_L}{Z_C}} \approx 1 - \sqrt{\frac{Z_L}{Z_C}}$$

$$\approx \frac{1}{1 + \frac{Z_L}{Z_0}}$$

$Z_L \rightarrow 0, Z_C \rightarrow \infty$

For k segments:

$$\frac{V_n}{V_0} = \left(1 - \frac{n \sqrt{z_l/z_c}}{n}\right)^n$$

$$\approx \exp\left[-n \sqrt{z_l/z_c}\right]$$

$$\approx \exp\left[\pm \frac{i\omega(\text{length})}{v}\right]$$

$$\begin{aligned} \sqrt{z_l z_c} &= \sqrt{i\omega g_l \mu l i\omega g_c \epsilon l} \\ &= \pm i\omega l \sqrt{\mu_0 \epsilon_0 \mu \epsilon} \\ &= \pm i\omega l \frac{1}{c} \text{const} \end{aligned}$$

$$\left(\frac{1}{\sqrt{\mu_0 \epsilon_0}} \times \frac{1}{\sqrt{\dots}}\right) \frac{1}{c} \text{ free space}$$

propagation of light up+down line
(both directions).

(2) Prop. both directions, \approx speed of light

$$\Leftrightarrow \alpha/\epsilon_r \text{ as } g_l g_c = 1, \mu r = 1$$

I bias

Application, connect wires to qubit



$$\Rightarrow T_1 = \frac{c}{\text{Re } \gamma(l\omega)}$$

$$= \frac{c}{\text{Re } (1/z_0)}$$

$$\approx c \cdot 50 \Omega$$

$$= 1 \text{ pF} \cdot 50 \Omega$$


$$= 50 \text{ pS}$$

→ Short coh. time
(even for big c)

(3) (Long) Wires look like π -lines (50Ω)

lots of dissip.

Termination of Lines

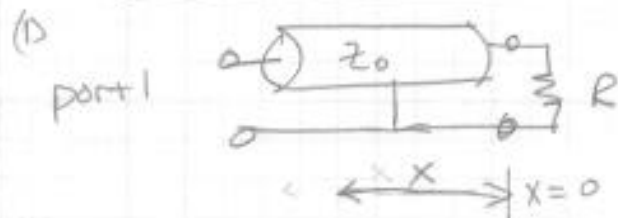

(2) 2 traveling waves

$$\begin{cases} \vec{V} = Z_0 \vec{I} e^{ikx} \\ \vec{V} = -Z_0 \vec{I} e^{-ikx} \end{cases} \quad k = \frac{\omega}{v}$$

↪ (-) because I changes direction

(3) Given \vec{V} (incident), what is \vec{V} (reflected)

$$S_{11} = \vec{V} / \vec{V} \quad (\text{Scatt. matrix})$$

(4) At $x=0$, conserve I at node

$$\vec{I} + \vec{I} = \frac{\vec{V} + \vec{V}}{R}$$

$$+ \begin{cases} \vec{V} = Z_0 \vec{I} \\ \vec{V} = -Z_0 \vec{I} \end{cases}$$

$$\vec{V}/Z_0 - \vec{V}/Z_0 = \vec{V}/R + \vec{V}/R$$

$$\vec{V} \left(\frac{1}{Z_0} - \frac{1}{R} \right) = \vec{V} \left(\frac{1}{Z_0} + \frac{1}{R} \right)$$



$$S_{11} = \vec{V} / \vec{V} = \frac{1 + Z_0/R}{1 - Z_0/R}$$

(5) $R=0$; $S_{11}=-1$; reflects to

$R=0$; $S_{11}=+1$; reflects to

* $R=Z_0$; $S_{11}=0$; matched; term. resistor absorbs pulse.

Finite z -lines — Resonators

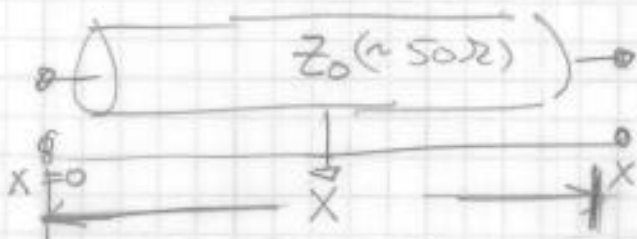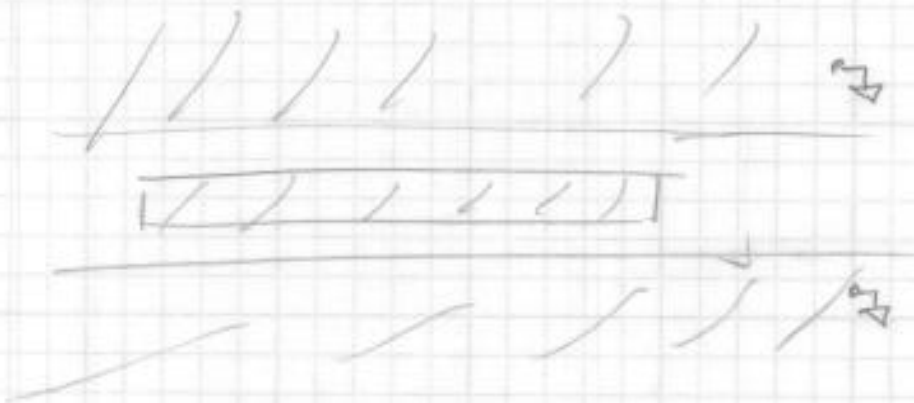

... can change direction

$$\vec{V} = -Z_0 \vec{I} e^{ikx}$$

$$\vec{V} = -Z_0 \vec{I} e^{-ikx}$$

Boundary Condition

B.C. At $x=0$, $I_{\rightarrow} - I_{\leftarrow} = 0$ (as open)

$$\Rightarrow \vec{I}(x) = I_0 (e^{ikx} - e^{-ikx}) \quad (I_0 \text{ a parameter})$$


$$= 2I_0 i \sin(kx)$$

$$Z = \frac{V}{I} = \frac{Z_0}{i} I_0 (e^{ikx} + e^{-ikx})$$

$$= 2Z_0 I_0 i \cos(kx)$$

$$Z = \frac{V}{I} = \frac{Z_0 \cos(kx)}{i \sin(kx)} = -i Z_0 \cot(kx)$$

imag. impedance (L or C, NOT R)


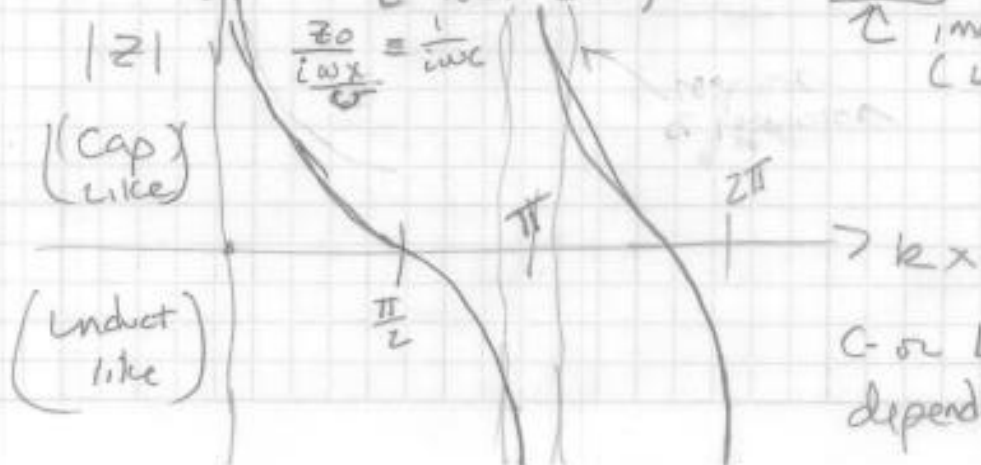


C- or L+ like depending on length.

What is resonance condition?

($Z = \infty$ for L/C)

For λ -line, happens when $kx = n\pi$

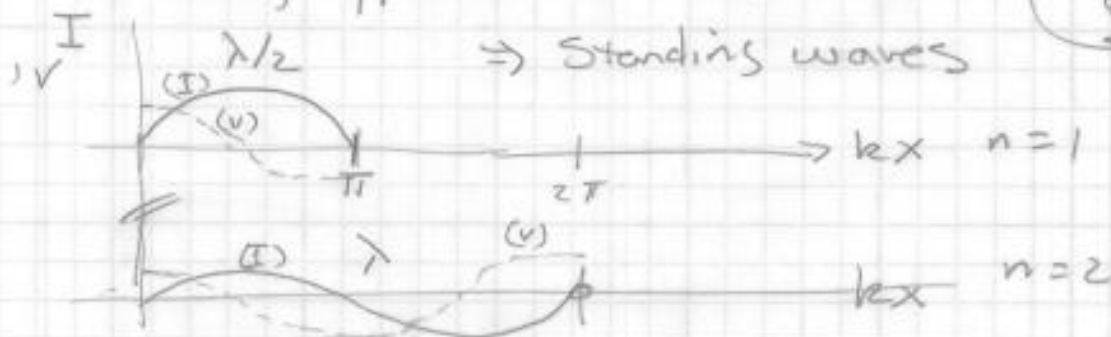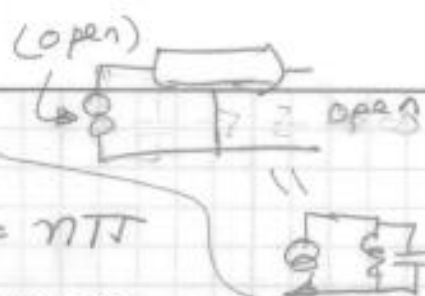

Around resonance $kx = \alpha_0 + \Delta\alpha$, $\alpha_0 = n\pi$

$$\frac{\cos(\alpha_0 + \Delta\alpha)}{\sin(\alpha_0 + \Delta\alpha)} \approx \frac{\cos\alpha_0 - \Delta\alpha \sin\alpha_0}{\sin\alpha_0 + \Delta\alpha \cos\alpha_0}$$

$$\approx \frac{1}{\Delta\alpha} \quad (\omega = \omega_{res} + \Delta\omega)$$

$$Z = \frac{-iZ_0}{i \frac{\Delta\omega}{\nu} x}$$

$$= \frac{Z_0}{i \Delta\omega \left(\frac{n\pi}{\omega_{res}} \right)}$$

$$= \frac{1}{i \Delta\omega \left(\frac{n\pi}{2\omega_{res} Z_0} \right)}$$


(LC model) $\equiv \frac{1}{i \Delta\omega C}$

$$\omega_{res} x = n\pi$$

effective cap
 $C = \left(\frac{n\pi}{2Z_0} \right) \frac{1}{\omega_{res}}$


$$\omega_{res}^2 = \frac{1}{LC}$$
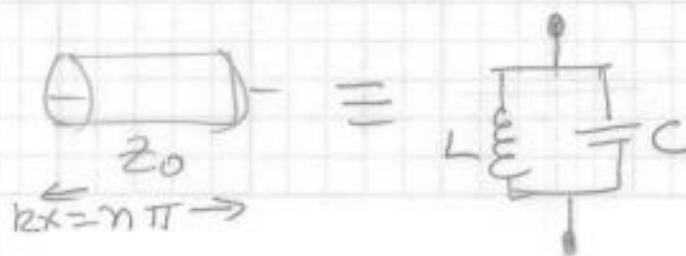
$$L = \frac{1}{C \omega_{res}^2} = \left(\frac{2Z_0}{n\pi} \right) \frac{1}{\omega_{res}}$$




Resonators


pancake (lumped element)

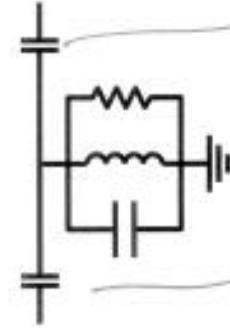

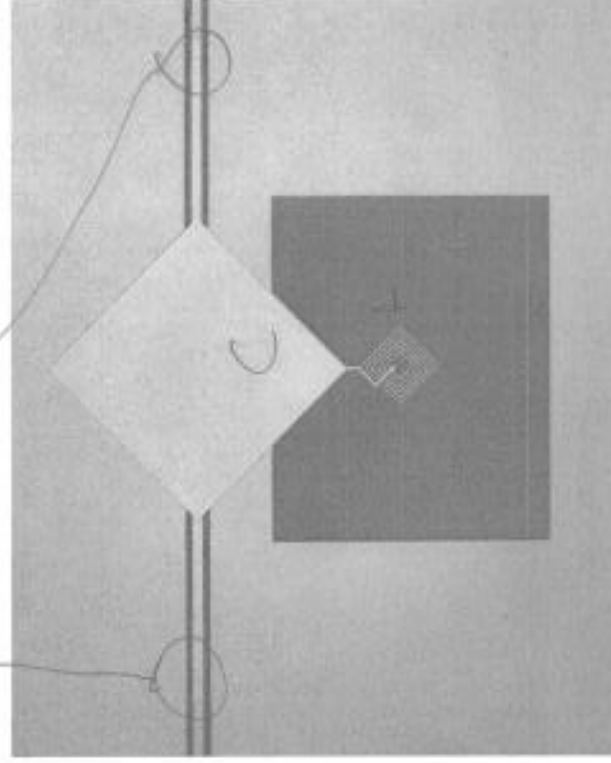
$C_c \sim 0.5\text{-}10\text{ fF}$
 $C \sim 5\text{ pF}$
 $L \sim 200\text{ pH}$
 $f_0 \sim 5\text{ GHz}$
 $Z_{\text{res}} \sim 10\ \Omega$





coplanar waveguide (CPW)

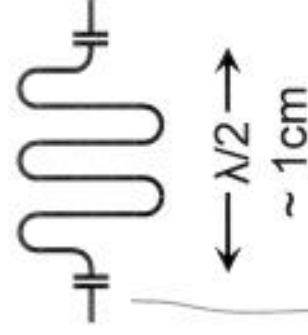

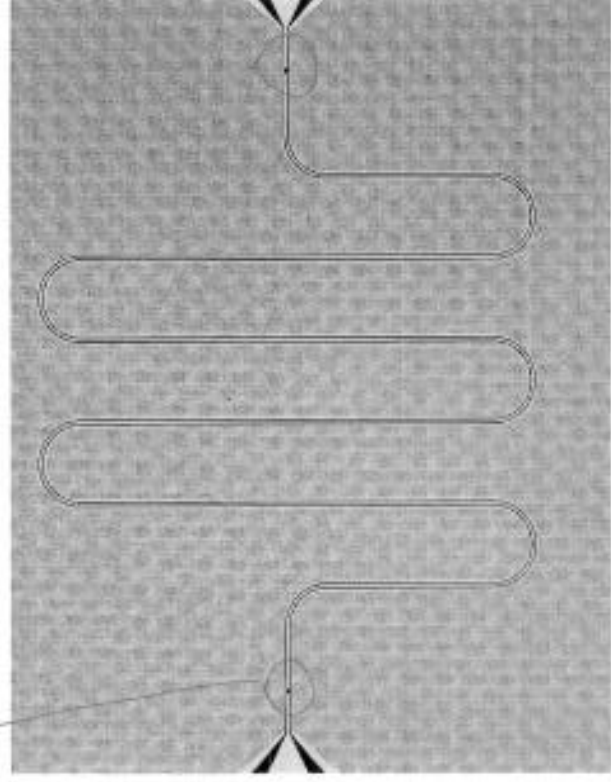
$C_c \sim 0.5\text{-}10\text{ fF}$
 $C \sim 150\text{ pF/m}$
 $L \sim 390\text{ nH/m}$
 $f_0 \sim 6\text{ GHz}$
 $Z_{\text{res}} \sim 50\ \Omega$



Experimental Setup

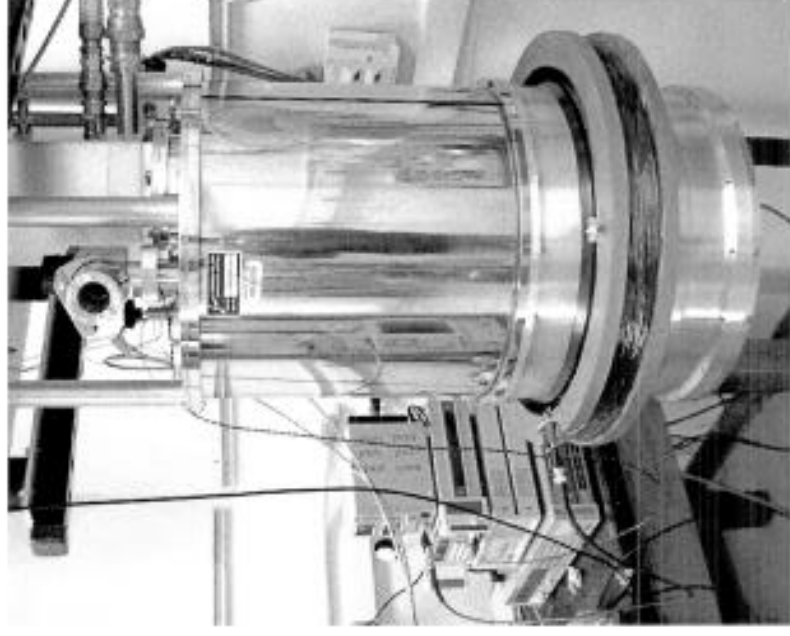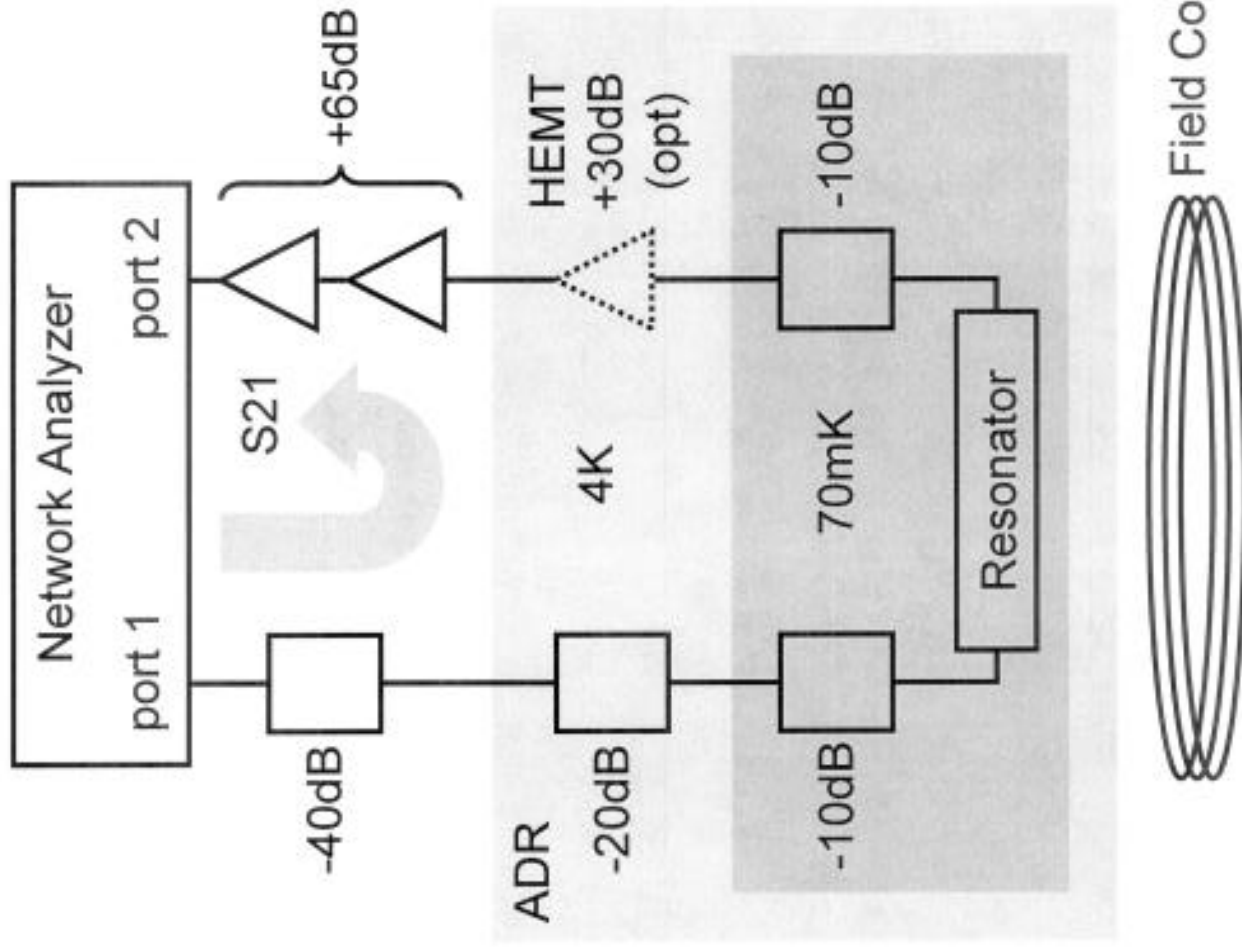




Microwave Resonator Measurements

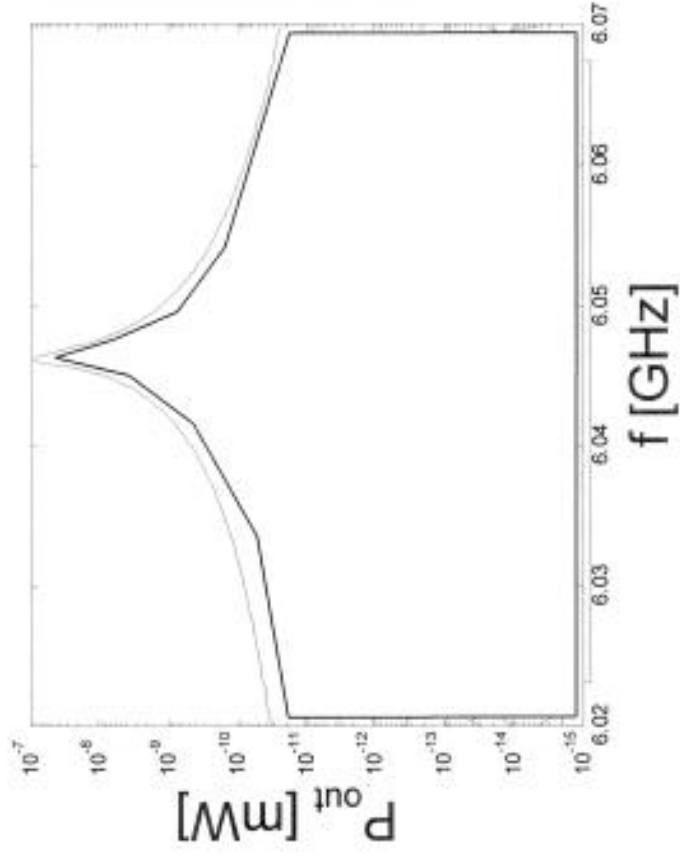

Let's do something Real circuit - (use these concepts!)

LC approx. of transm. line; Real Circuit

show
pics

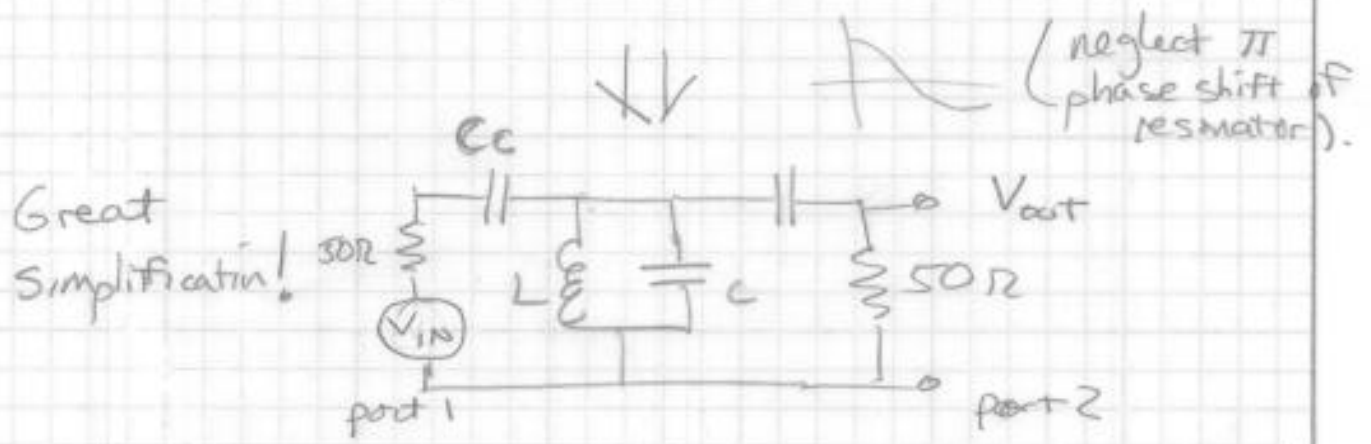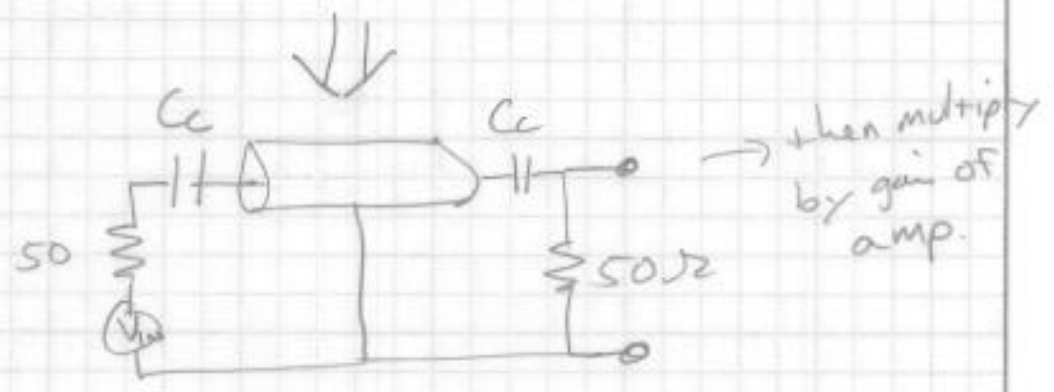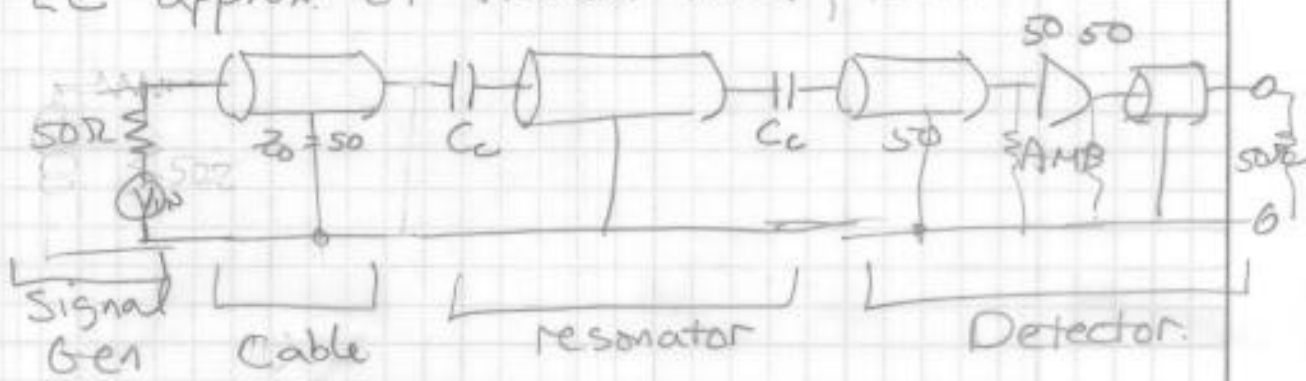

What is $\frac{V_{out}}{V_{in}} = S_{21}$? ← Scattering Matrix
 Wave in port 1
 Wave out port 2


Circuit Analysis

Imppt. Simplification $|Z_{cc}| = \left| \frac{1}{i\omega C_c} \right| \gg R = 50 \Omega$

(C_c couples resonator to outside world, but want to couple weakly so only slightly perturbs resonator)

2 steps:

(1) Z transf.

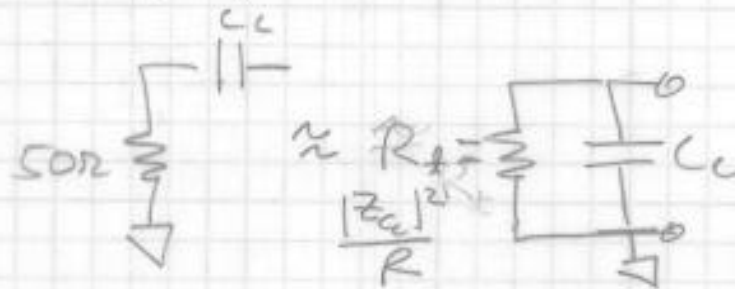

$$Z = R + \frac{1}{i\omega C_c}$$

$$\text{Re } Y = \frac{R}{R^2 + |Z_{cc}|^2}$$

$$Y = \frac{1}{Z} = \frac{1}{R + \frac{1}{i\omega C_c}}$$

$$= \frac{R - \frac{1}{i\omega C_c}}{R^2 + |Z_{cc}|^2}$$


$$\approx \frac{R}{|Z_{cc}|^2} + i\omega C_c$$

transf R Same Cap



$$R_x = \frac{1}{\text{Re}(Y)} = \frac{|Z_{cc}|^2}{R}$$

$$\approx \frac{R}{|Z_{cc}|^2}$$

(2) Thev. Equiv. Source:

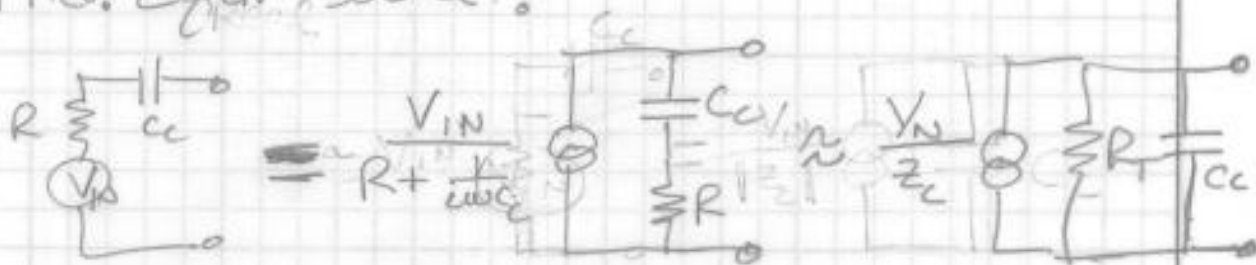

New Circuit:

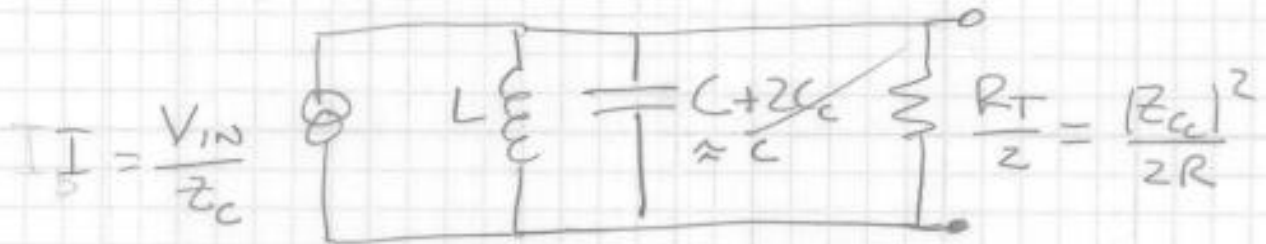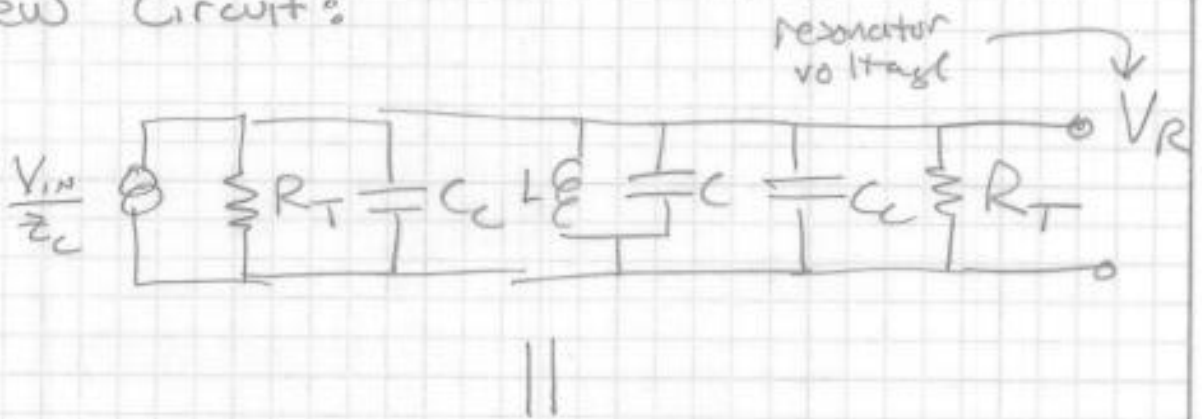

Just a L-C-R circuit, analyzed previously.

$$V_J = Z I \quad \omega = \omega_{res} + \Delta\omega, \quad \omega_{res} = \sqrt{\frac{1}{L(C+2Z_C)}}$$


near resonance $\approx \frac{1}{z_c \Delta\omega C + \frac{1}{R_T/z_c}} \frac{V_{IN}}{Z_C}$

What is preamp voltage (not just reson. V_J)?



$$V_{out} = \frac{R}{R + z_c} V_J \approx \frac{R}{z_c} V_J$$
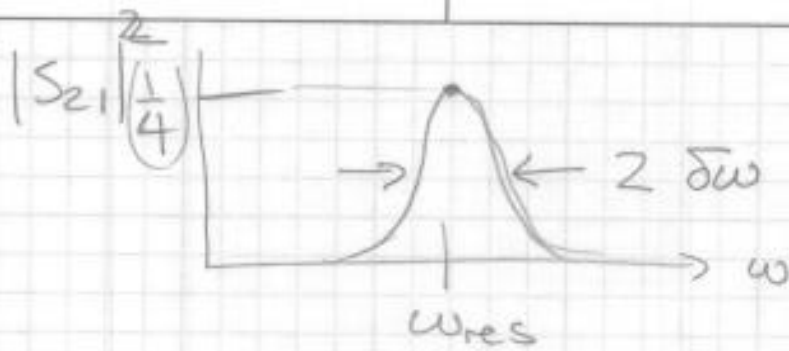
$$S_{z1} = \frac{V_{out}}{V_{IN}} = \frac{R}{z_c^2} \frac{1}{z_c \Delta\omega C + \frac{z_c}{R_T}} = \frac{1}{z_c} \frac{R R_T}{z_c^2} \frac{1}{i \Delta\omega C R_T + 1} = \frac{1}{z_c} \frac{1}{i \Delta\omega (C R_T) + 1}$$



On resonance, $\Delta\omega = 0$, $S_{21} = \frac{1}{2}$

FWHM (power) when $\Delta\omega C R_T = 1$
 $\Delta\omega = \delta\omega/2$

$$\delta\omega = \frac{2}{C R_T}$$

$$= \frac{1}{C(R_T/2)} \text{ ; normal formula for } Q.$$

Makes sense, on resonance, circuit sends power thr. resonator



$$V_{out} = \frac{V_{IN}}{2}$$

(but circuit phase shifts by π)

Summary: Small C_c impedance transforms


$$R \approx 50\Omega \text{ to } \frac{|Z_c|^2}{R} \approx 10^6\Omega$$

Thus resonator not damped much.

HW problem for making high-R I-source:



Josephson Junction Decoherence

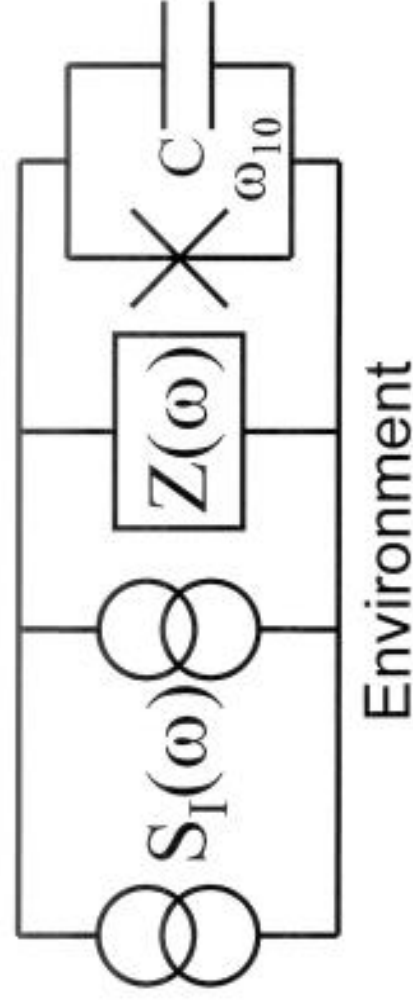


$$\begin{aligned}
 H_{(2)} = & \sigma_x \bullet I_{JWC}(t) \bullet (\hbar / 2\omega_{10} C)^{1/2} / 2 \\
 & + \sigma_y \bullet I_{JWS}(t) \bullet (\hbar / 2\omega_{10} C)^{1/2} / 2 \\
 & + \sigma_z \bullet \delta I_{dc}(t) \bullet (\partial E_{10} / \partial I_{dc}) / 2
 \end{aligned}$$

Spontaneous Emission
(decay $1 \rightarrow 0$)

Noise at ω_{10} (σ_x, σ_y op.'s)

Noise at LF (σ_z op.'s)

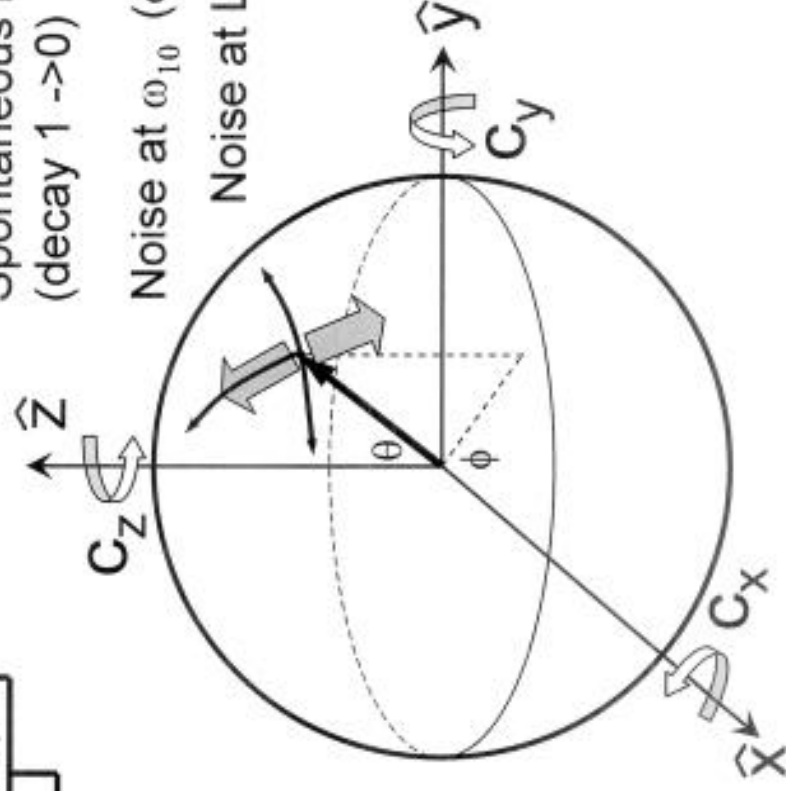

Decoherence arises from
noise and dissipation

Decoherence from noise (need more gen. model than $1 \rightarrow 0$)

- (1) Density Matrix Approach (standard, won't talk about)
- Ensemble avg, good for NMR, we use
 - Only treats rates (like T_1) exp. decay.
 - Not good for correl. noise (like we have)

relax results

(2) Noise in Bloch vector (most physical)

- can treat correl noise
- Similar to treating noise in electrical circuits
- Full thx, use with "quantum Monte Carlo/jumps"
(Not go into here, but readily generalized)
(Just need to add T_1 , energy decay)

Noise Theory:

IF control signals change B.V., then
noise in control signal gives noise in B.V.!

<u>Spin</u> :	Z	B_z	low DC (low Freq)
	X, Y	B_x, B_y	HF (Transid. Freq)
ϕ qubits:	Z	I	DC
	X, Y	I	HF

→ Concerned about noise in bias I.

Noise

Energy Decay From Dissip; $1 \rightarrow 0$. "T," state decay.
 Can also have $1 \leftrightarrow 0$, dephasing from noise.
 1st, need to describe noise.

$I(t)$  Random Fluctuations of I (or V)
 Assume comes from sum of sine & cosine waves

$$I(t) = \sum_F \{ S_F \sin(2\pi Ft) + C_F \cos(2\pi Ft) \}$$

\uparrow Random Amp's + Phases
 \uparrow Random



$$\langle I^2 \rangle = \frac{1}{2} \sum_F \{ (S_F)^2 + (C_F)^2 \}$$

Incoherent Sum (of Power)
since $\langle \sin^2 \rangle = \langle \cos^2 \rangle = 1/2$

Diff. F \perp

$\{ (S_F)^2 + (C_F)^2 \}$ gives a spectral density, noise as a function of freq.

To meas.

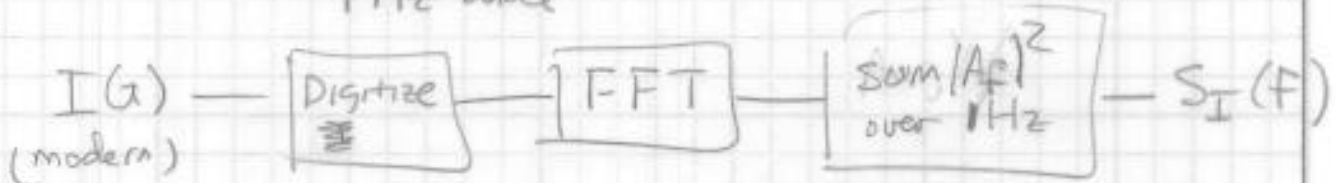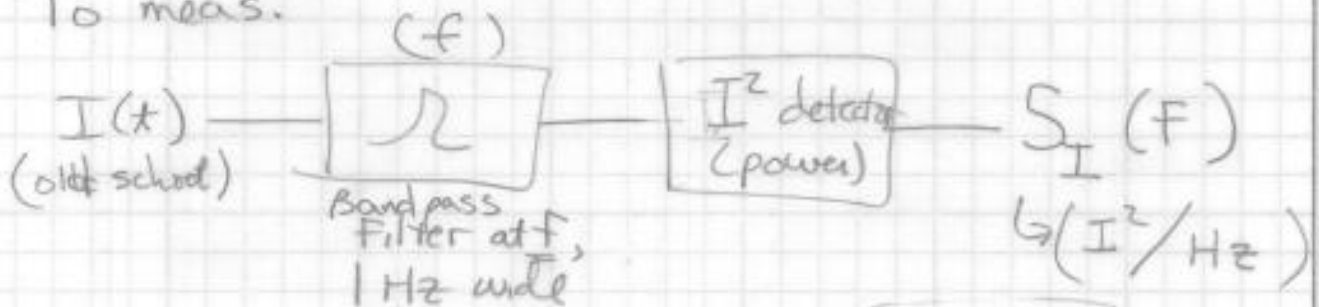

Note: With classical noise, only makes sense to discuss noise at (+) Freq. only (No LF filters!).

$$\langle I^2 \rangle = \int_0^{\infty} S_I(f) df$$


If want to know time correlation of noise, Wiener-Kinchine theorem (not derived here)

$$\langle I(t) I(0) \rangle = \int_0^{\infty} df S_I(f) \cos 2\pi f t$$

(t -Correl. = FT of $S_I(f)$)
($t=0$ is top eqn), Total Noise

Example: White noise; $S_I(f) = \text{const.}$

Resistor noise

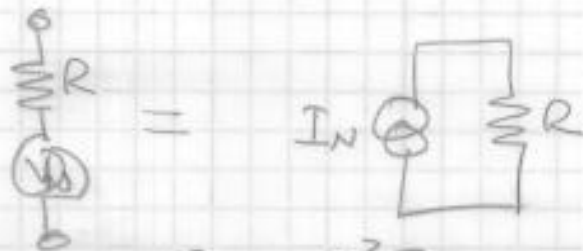

$$S_{V_N} = R^2 S_{I_N}$$

$$S_{I_N} = \frac{4kT}{R} \quad (\text{classical})$$

FT of const is δ function,

so noise uncorrelated in time.

[Computer simulation; take each $I_N(t)$ randomly
or Random Amps in f , then F.T.]

Phase Noise (Z) (consider $|0\rangle + |1\rangle$ state $e^{i\phi}$)

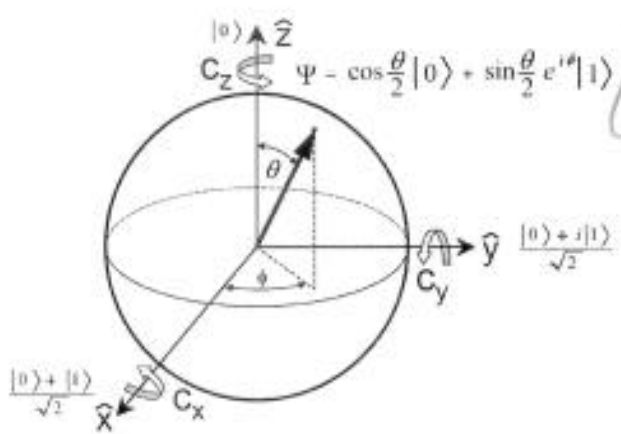


FIG. 2. Bloch sphere representation of the qubit state. Control vector $c = (c_x, c_y, c_z)$ rotates the Bloch vector around axis of direction $c_x \hat{x} + c_y \hat{y} + c_z \hat{z}$ with angle $|c|$.

and $I_j(t)$. If these control currents have constant values over time Δt , we can define a control vector $\vec{c} = (c_x, c_y, c_z)$ with

$$\vec{c} = \left(I_{\mu x} \sqrt{\frac{\hbar}{2\omega_{10} C}}, I_{\mu y} \sqrt{\frac{\hbar}{2\omega_{10} C}}, I_{\mu z} \sqrt{\frac{\hbar}{2\omega_{10} C}} \frac{\partial E_{10}}{\partial I_{dc}} \right) \frac{\Delta t}{\hbar}. \quad (6)$$

The control currents change the qubit state after time Δt according to the unitary transformation

$$U = \exp[-iH_{(2)}\Delta t/\hbar], \quad (7a)$$

$$= \exp[-i\hat{\sigma} \cdot \vec{c}/2], \quad (7b)$$

$$= \hat{\sigma}_0 \cos \frac{|c|}{2} - i \frac{\hat{\sigma} \cdot \vec{c}}{|c|} \sin \frac{|c|}{2}, \quad (7c)$$

where $\hat{\sigma} = (\hat{\sigma}_x, \hat{\sigma}_y, \hat{\sigma}_z)$ and $\hat{\sigma}_0$ is the identity matrix.

One way to visualize how \vec{c} controls the qubit state is via the standard Bloch-sphere description. As illustrated in Fig. 2, the direction of the Bloch vector describes the qubit state according to $\Psi = \cos(\theta/2)|0\rangle + \sin(\theta/2)\exp(i\phi)|1\rangle$. The angle θ of the vector corresponds to the occupation amplitude of the state, whereas the angle ϕ gives the phase of the state. The probability of measuring the ground state is given by $\cos^2(\theta/2)$. Operations of $\hat{\sigma}_x$, $\hat{\sigma}_y$, and $\hat{\sigma}_z$ correspond to rotations of the state vector around the x , y , and z axis, respectively. In general, a control vector \vec{c} rotates the Bloch vector around the \vec{c} axis with angle $|c|$. For example, a " $\pi/2$ -pulse" with control vector $\vec{c} = (0, \pi/2, 0)$ changes the state $|0\rangle$ to the state $(|0\rangle + |1\rangle)/\sqrt{2}$.

III. CALCULATION OF DECOHERENCE FOR AN ARBITRARY NOISE SOURCE

Because the bias current controls the qubit, noise in the bias current fluctuates the qubit state and causes decoherence. In this section we calculate how noise randomly rotates the Bloch vector around the three axes. Because we separated the effect of the bias current into low $I_j(t)$ and microwave frequency $I_{\mu x}(t)\cos\omega_1 t + I_{\mu y}(t)\sin\omega_1 t$ components, the effect of noise can be separated likewise. Since the

net effect of these rotations depends on the state of the qubit, we calculate how these fluctuations affect the measurement of the state for two typical experimental situations.

Current noise at low frequency fluctuates the c_z component of the control vector, which randomly rotates the Bloch vector around the z axis due to $\hat{\sigma}_z$ operations. These random rotations produce noise in the phase ϕ of the qubit state. Since the phase is $\phi(t) = \int_0^t dt' \omega_1(t')$, the phase noise after a time t is

$$\phi_n(t) = \frac{\partial \omega_{10}}{\partial I_{dc}} \int_0^t dt' I_n(t'). \quad (8)$$

Physically, phase noise arises from noise current flowing through the nonlinear inductance of the junction that in turn causes ω_{10} to vary.

The magnitude of the phase noise is described by its mean-squared value $\langle \phi_n^2(t) \rangle$. This quantity is calculated with the noise power of I_n , described as the spectral density $S_I(f)$. It is defined as the mean-squared amplitude of the current noise at frequency f per 1 Hz bandwidth. The time average of the correlation function is computed with the noise power by

$$\langle I_n(t)I_n(0) \rangle = \int_0^\infty df S_I(f) \cos 2\pi ft. \quad (9)$$

Using Eq. (8) the mean-squared phase noise is

$$\langle \phi_n^2(t) \rangle = \left(\frac{\partial \omega_{10}}{\partial I_{dc}} \right)^2 \left\langle \left(\int_0^t dt' I_n(t') \right)^2 \right\rangle \quad (10a)$$

$$= \left(\frac{\partial \omega_{10}}{\partial I_{dc}} \right)^2 \int_0^\infty df S_I(f) \int_0^t dt' \int_0^t dt'' \text{Re} e^{i2\pi f(t'-t'')} \quad \text{sp. out} \quad (10b)$$

$$= \left(\frac{\partial \omega_{10}}{\partial I_{dc}} \right)^2 \int_0^{\omega_{10}/2\pi} df S_I(f) W_0(f), \quad (10c)$$

where $W_0(f)$ is a spectral weight function given by

$$W_0(f) = \left| \int_0^t dt' e^{i2\pi ft'} \right|^2 \quad (11a)$$

$$= \frac{\sin^2(\pi ft)}{(\pi f)^2} \rightarrow \frac{(\pi ft)^2}{(\pi f)^2} \quad (11b) \rightarrow t^2$$

The phase noise integral is cutoff for frequencies greater than $\omega_{10}/2\pi$. For these frequencies, the noise current primarily flows through the junction capacitance, not the junction, and thus does not significantly modulate ω_{10} . Furthermore, noise at ω_{10} should not be included because it is accounted for in stimulated transitions, as computed below. Integrating the noise to a cutoff frequency $\omega_{10}/2\pi$ is a good approximation because for most circuit impedances a change in this cutoff frequency only logarithmically affects the phase noise [see Eq. (26)].

Flucts in ϕ

$\langle \phi_n \rangle = 0$

$\langle I^2 \rangle = \int_0^\infty df S_I(f)$

using ωX

t^2 complex conj.



White noise




$$\langle \phi_N^2 \rangle = \left(\frac{\partial w_0}{\partial I} \right)^2 S_F^0 \int_0^\infty \frac{d(mF)}{(\pi m)} \frac{\sin^2(\pi F t)}{(\pi F t)^2} \frac{1}{t^2}$$

$$= \left(\frac{\partial w_0}{\partial I} \right)^2 S_F^0 \frac{t}{\pi} \int_0^\infty \frac{\sin^2 y}{y^2} dy \Big|_{-\infty}^{\infty} = \pi$$

$\langle \phi_N^2 \rangle \propto t$; like diffusion! $= \left(\frac{\partial w_0}{\partial I} \right)^2 S_F^0 t$

1/F noise

(more physical, ϕ, Φ, I_0 fluct.)

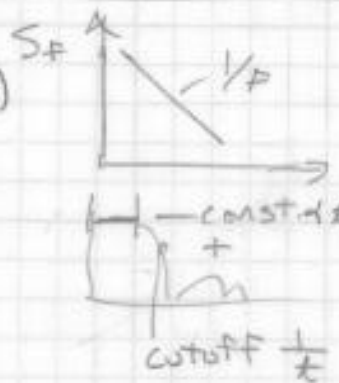

$$\langle \phi_N^2 \rangle = \left(\frac{\partial w_0}{\partial I} \right)^2 \int_0^\infty dF \frac{S_I^*(1\text{Hz})}{f} \frac{\sin^2(\pi F t)}{(\pi F)^2}$$

$$\approx \left(\frac{\partial w_0}{\partial I} \right)^2 S_I^* \int_0^\infty \frac{dF}{F} \Big|_{-\infty}^{\infty} \approx \left(\frac{\partial w_0}{\partial I} \right)^2 S_I^*(1\text{Hz}) \ln \left(\frac{0.401}{F_m t} \right) t^2$$

$$\equiv \left(\frac{t}{t_{1/4}} \right)^2 \text{ (line of exp)}$$

$\langle \phi_N^2 \rangle \propto t^2$, makes sense!

LF ($\frac{1}{F}$) noise; bias fluctuates very slowly, different $w_{i0} + \delta w_{i0}$ each experiment; $\phi_N \propto \int_0^t \delta w_{i0} dt \propto t$

so $\phi_N^2 \propto t^2$.


X, Y errors from H.F. Noise

$$I = I_{LF}(t) + I_c(t) \cos \omega_0 t + I_s(t) \sin \omega_0 t$$



$$H = \frac{\sigma_z}{2} \left(\frac{\partial \omega_0}{\partial I} \right) I_{LF}(t) + \frac{\sigma_x}{2} \frac{1}{\sqrt{2\epsilon_0 c}} I_c(t) + \frac{\sigma_y}{2} \frac{1}{\sqrt{2\epsilon_0 c}} I_s(t)$$

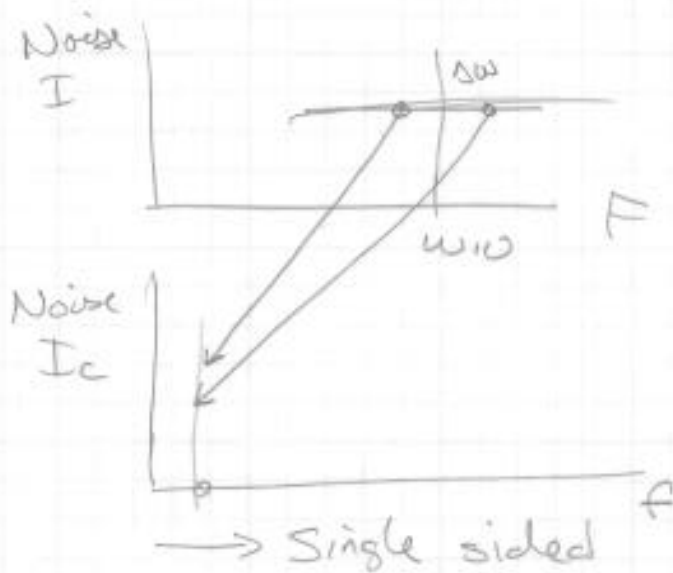Need to express H.F. noise around ω_0 as noise in $I_c(t)$, $I_s(t)$



Noise at $\pm \Delta\omega$ mixes to same freq. $\Delta\omega$

$$S_{I_c} = S_{I_s} = 2 S_{\pm}(\omega_0/2\pi)$$

since assume noise const. around $\omega_0/2\pi$


Noise Mixing

$$\begin{aligned} I_N &= \sum_{\pm\Delta\omega} c_{\Delta\omega} \cos(\omega_{10}t + \Delta\omega t) + s_{\Delta\omega} \sin(\omega_{10}t + \Delta\omega t) && \text{Noise from } +\text{- } \Delta\omega \text{ around } \omega_{10} \\ &= \sum_{\pm\Delta\omega} c_{\Delta\omega} [\cos(\omega_{10}t) \cos(\Delta\omega t) - \sin(\omega_{10}t) \sin(\Delta\omega t)] + s_{\Delta\omega} [\sin(\omega_{10}t) \cos(\Delta\omega t) + \cos(\omega_{10}t) \sin(\Delta\omega t)] \\ &= \cos(\omega_{10}t) \sum_{\Delta\omega} \{(c_{+\Delta\omega} + c_{-\Delta\omega}) \cos(\Delta\omega t) + (s_{+\Delta\omega} - s_{-\Delta\omega}) \sin(\Delta\omega t)\} + \sin(\omega_{10}t) \sum_{\Delta\omega} \dots \end{aligned}$$

Noise adds from $+\Delta\omega$ and $-\Delta\omega$

Θ errors from noise in mw drive

I_c, I_s white noise

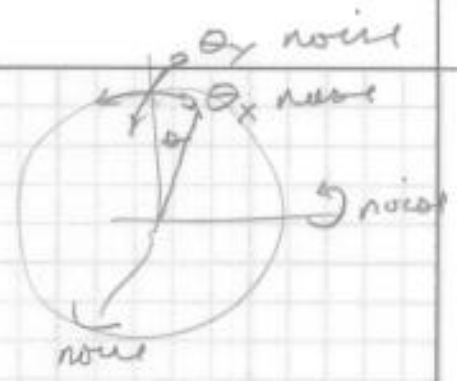

$$\langle \Theta_x^2 \rangle = \frac{1}{2\pi\omega_0 C} 2 S_I(\omega_0/2\pi) t$$

$$= \langle \Theta_y^2 \rangle$$

(just like noise in z , charge constants)

Total tilt Θ of B.V. is (Starting from $|0\rangle$ state (at top))

$$\langle \Theta^2 \rangle = \langle \Theta_x^2 \rangle + \langle \Theta_y^2 \rangle$$

$$= \frac{1}{2\pi\omega_0 C} 4 S_I t$$

Ampl $|0\rangle = \cos(\Theta/2)$

$$P_0 = \langle \cos^2(\Theta/2) \rangle = \langle \left[1 - \frac{1}{2} \left(\frac{\Theta}{2} \right)^2 \right]^2 \rangle$$

$$\approx \langle 1 - 2 \left(\frac{\Theta}{2} \right)^2 \rangle$$

$$= 1 - \frac{1}{4} \langle \Theta \rangle^2$$

$$= 1 - \frac{1}{2\pi\omega_0 C} S_I \left(\frac{\omega_0}{2\pi} \right) t$$

↳ Represents transition rate γ_N of $0 \rightarrow 1$

Likewise, if start at bottom $|1\rangle$;

$\gamma_N =$ same as above.



ϕ_N and Ramsey Sequence

How to meas ϕ_N ?

γ_N meas. from $|0\rangle$ or $|1\rangle$ state



With Ramsey seq.

$\langle \phi_N^2 \rangle$ seen as noise in angle θ_x

$\langle \theta_y^2 \rangle$ " " " " angle θ_y

$\langle \theta_x^2 \rangle$ not seen!

$$P_0 = 1 - \frac{1}{4} \langle \theta_y^2 \rangle - \frac{1}{4} \langle \phi_N^2 \rangle$$

$$= 1 - \frac{1}{2} \gamma_N t - \frac{1}{4} \langle \phi_N^2 \rangle$$

$\frac{1}{2}$ as his because

only 1 component of μ wave noise.

Beyond small angle expansion of θ^2 -

Many modes of noise \Rightarrow Gaussian Distribution

$$\frac{dp(x)}{dx} = \frac{e^{-x^2/2\langle x^2 \rangle}}{\sqrt{2\pi\langle x^2 \rangle}}$$

$$\text{So } P_0 = \int_{-\infty}^{\infty} d\theta \frac{e^{-\theta^2/2\langle \theta^2 \rangle}}{\sqrt{2\pi\langle \theta^2 \rangle}} \cos^2(\theta/2)$$

$$= \frac{1}{2} + \frac{1}{2} \exp\left[-\frac{\langle \theta^2 \rangle}{2}\right]$$

Thus $P_0 = \frac{1}{2} + \frac{1}{2} \exp\left[-\frac{\langle \theta^2 \rangle}{2}\right]$ $\left[\frac{1}{2} \text{ also found in transition picture} \right]$
 $0 \leftrightarrow 1$ transitions cause avg to $\frac{1}{2}$
 and dephasing

$$\begin{aligned}
 \gamma_N \quad \langle \theta^2 \rangle & \langle \phi_p^2 \rangle & P_0 &= \frac{1}{2} + \frac{1}{2} \exp \left[-\frac{1}{2k\omega_0 c} 2S_I t / 2 \right] \\
 & & &= \frac{1}{2} + \frac{1}{2} \exp \left[-\gamma_N t \right]
 \end{aligned}$$

$$\begin{aligned}
 \phi_N \quad P_0 &= \frac{1}{2} + \frac{1}{2} \exp \left[-\langle \phi_p^2 \rangle / 2 \right] \\
 (1/F) \rightarrow & = \cancel{\frac{1}{2} + \frac{1}{2} \exp \left[-\left(\frac{\partial \omega_0}{\partial I} \right)^2 S_I \ln \left(\frac{1}{2} \right) t^2 \right]} \\
 & \equiv \frac{1}{2} + \frac{1}{2} \exp \left[-\frac{1}{2} (t/t_F)^2 \right]
 \end{aligned}$$

Combining both (as non-correlated)

$$P_0 \approx \frac{1}{2} + \frac{1}{2} \exp \left[-\gamma_N t \right] \exp \left[-\frac{1}{2} \left(\frac{t}{t_F} \right)^2 \right]$$

Multiply decay from both sources.

Dissipation and Noise

(1) Up to now, treated separately: But can be combined!

Idea: Classical current $\sim \cos \omega t = \frac{e^{i\omega t} + e^{-i\omega t}}{2}$


has $\pm \omega$ freq. components

Quantum states differ by $e^{-i\omega_0 t}$ factor,
 so $\pm \omega$ represents \pm energy transitions

* Thus, dissip. repres. by diff noise \pm freq's!


(2) How treat dissip in Q.M. since Q.M. reversible?

Std. - Fermi
 Golden
 Rule

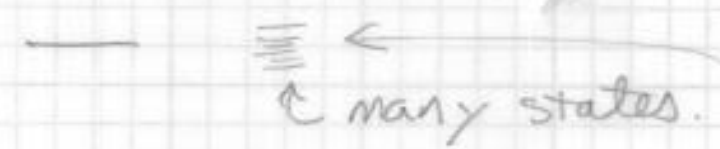

Small coupling to many states
 Energy/State never comes back.

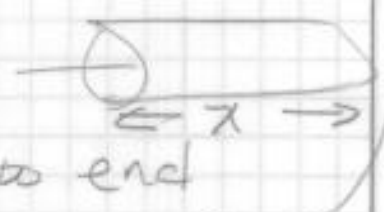• Example was in t -line,
 where line $\rightarrow \infty$ means
 energy reflected back to end




* Model for a resistor: by both of
 finite length λ ; can describe $\sqrt{L-C}$ modes
 let $\lambda \rightarrow \infty$ or as density of modes.

Reson: $\omega_n = n \left(\frac{\pi v}{\lambda} \right) \equiv n \omega_0$

$$C_n = \frac{1}{n} \frac{\pi}{2Z_0} \frac{1}{\omega_n}$$

$$= \left(\frac{\pi}{2Z_0} \right) \frac{1}{\omega_0}$$

$$= \text{const.}$$

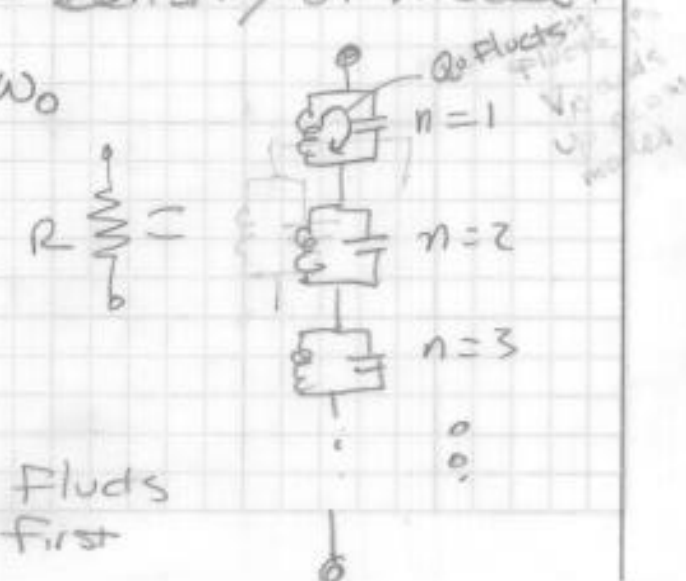

With Series circuit, V_n Flucts
 add up \rightarrow Calc. that first

To compute noise ($\pm \omega$); look at correlator

← now operators

$$\langle \hat{V}(t) \hat{V}(0) \rangle = \frac{\langle \hat{Q}(t) \hat{Q}(0) \rangle}{C^2}$$

$$\hat{Q}(t) = \frac{\sqrt{2\hbar\omega_n C}}{2} (a e^{-i\omega_n t} + a^\dagger e^{i\omega_n t})$$

(For 1 mode)
res. freq. ω_n)

$$= \frac{2\hbar\omega_n C}{4C^2} \langle (a e^{-i\omega_n t} + a^\dagger e^{i\omega_n t})(a - a^\dagger) \rangle$$

$$= \frac{\hbar\omega_n}{2C} \left[\langle a a^\dagger \rangle e^{-i\omega_n t} + \langle a^\dagger a \rangle e^{i\omega_n t} + \langle a a \rangle_0 - \langle a^\dagger a^\dagger \rangle_0 \right]$$

$$\langle a^\dagger a \rangle \neq \langle a a^\dagger \rangle = \langle a^\dagger a \rangle + 1$$

Something interesting \rightarrow non classical
 $\pm \omega_n$ spectral weight!

For H.O. state (bosonic mode), temp. T

$$\langle a^\dagger a \rangle_T = \frac{1}{e^{\hbar\omega_n/kT} - 1} \rightarrow 0 \text{ with } T \rightarrow 0$$

$$\langle a a^\dagger \rangle_T = \frac{1 + (e^{\hbar\omega_n/kT})}{e^{\hbar\omega_n/kT} - 1} \rightarrow 1 \text{ with } T \rightarrow 0$$

$$= \frac{1}{1 - e^{-\hbar\omega_n/2T}}$$


Only $e^{-i\omega_n t}$
freq. content

$$\langle \hat{V}(t) \hat{V}(0) \rangle = \sum_n \frac{\hbar \omega_n}{2 \left(\frac{\pi}{2z_0} \frac{1}{\omega_0} \right)} \left[\frac{1}{e^{\hbar \omega_n / kT} - 1} e^{-i\omega_n t} - \frac{1}{e^{-\hbar \omega_n / kT} - 1} e^{i\omega_n t} \right]$$

total (sum over all modes) const

$$= \frac{z_0}{\pi} \sum_n \omega_0 \left[\frac{\hbar \omega_n}{e^{\hbar \omega_n / kT} - 1} e^{-i\omega_n t} + \frac{-\hbar \omega_n}{e^{-\hbar \omega_n / kT} - 1} e^{i\omega_n t} \right]$$

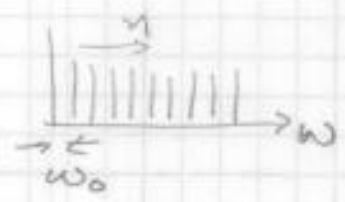$\int_0^\infty d\omega$ $+ \omega_n \rightarrow -\omega_n$



$$= 2z_0 \int_{-\infty}^{\infty} d\left(\frac{\omega}{2\pi}\right) \left[\frac{\hbar \omega}{1 - e^{-\hbar \omega / kT}} e^{+i\omega t} \right]$$


$z_0 = \text{resistance}$ \hookrightarrow Now 2-sided integral

* Now F.T. both sides

$$S_V^{\text{pu}}\left(\frac{\omega}{2\pi}\right) = 2z_0 \frac{2\hbar \omega}{1 - e^{-\hbar \omega / kT}} \quad \text{+ and - frequencies!}$$

General case for z

$$S_I^{\text{qu}} = S_V / |z|^2 = \text{Re}\{z\} \frac{2\hbar \omega}{1 - e^{-\hbar \omega / kT}} \quad \text{Re}\left(\frac{z}{|z|^2}\right) = \text{Re}\left(\frac{z}{z z^*}\right) = \text{Re}\left(\frac{1}{z^*}\right)$$

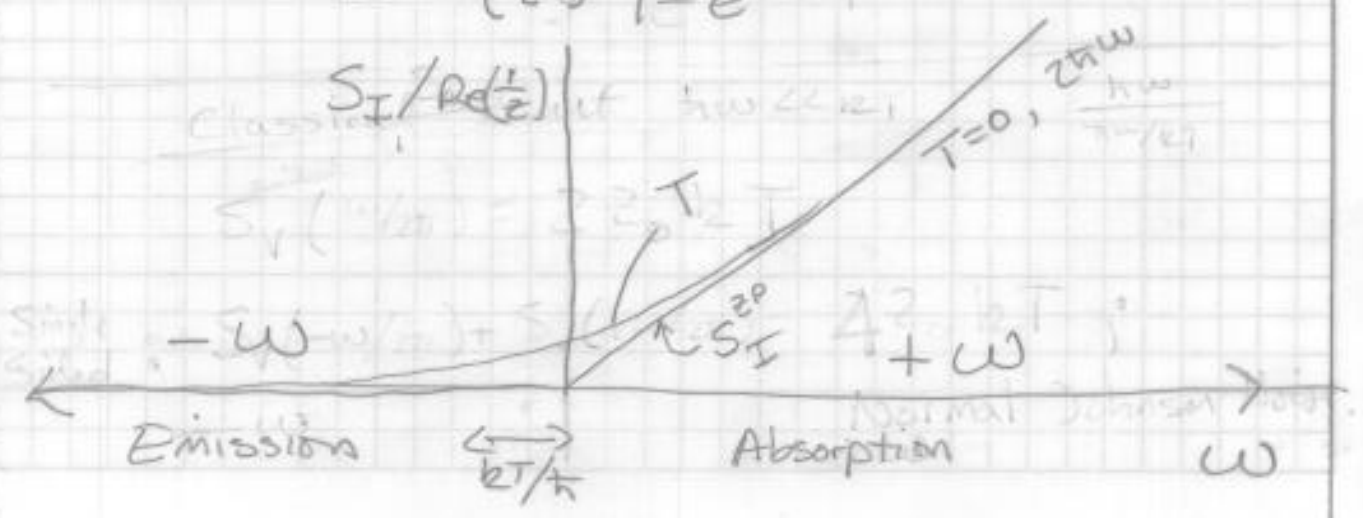

Physics of Spectrum.

(0) Absorption = $+\omega$ } $\hat{V}(t) \propto a e^{-i\omega t} + a^\dagger e^{i\omega t}$
 Emission = $-\omega$ } $\underbrace{a}_{\text{emit photon}} \quad \underbrace{a^\dagger}_{\text{absorb photon}}$

① Emission = $-\omega$ = Blackbody Formula (10)

② $S_I^{\pm p}(\omega/2\pi) = S_I^{\text{qu}}(+\omega/2\pi) - S_I^{\text{qu}}(-\omega/2\pi)$ Diff. of spec

$$= 2 \operatorname{Re}\left(\frac{1}{\epsilon}\right) \left[\frac{\hbar\omega}{1 - e^{-\hbar\omega/kT}} - \frac{-\hbar\omega}{1 - e^{+\hbar\omega/kT}} \right]$$

$$= 2 \operatorname{Re}\left(\frac{1}{\epsilon}\right) \hbar\omega \left[\langle a a^\dagger \rangle - \langle a^\dagger a \rangle \right]$$

$$= \operatorname{Re}\left(\frac{1}{\epsilon}\right) 2\hbar\omega$$

(Same Calc., only use $+\omega$)

$\gamma_1 = \gamma_N (S_I \leftarrow S_I^{\text{zp}}(\omega_0/2\pi))$


$$= \frac{1}{2\hbar\omega_0 c} 2\hbar\omega_0 \operatorname{Re}\left(\frac{1}{\epsilon}\right)$$

$= \frac{1}{c} \operatorname{Re}\left(\frac{1}{\epsilon}\right)$; Dissipation Formula Derived previously

* Z.P. Flucts. drive $1 \rightarrow 0$ transition (dissipation)

$$\begin{cases} S_I^{\text{qu}}(-\omega/2\pi) - \text{Classical Noise } 0 \leftrightarrow 1 (\gamma_N) \\ S_I^{\text{zp}}(+\omega/2\pi) - \text{Z.P. Noise } 1 \rightarrow 0 (\gamma_1) \end{cases}$$

② Two ways to picture noise

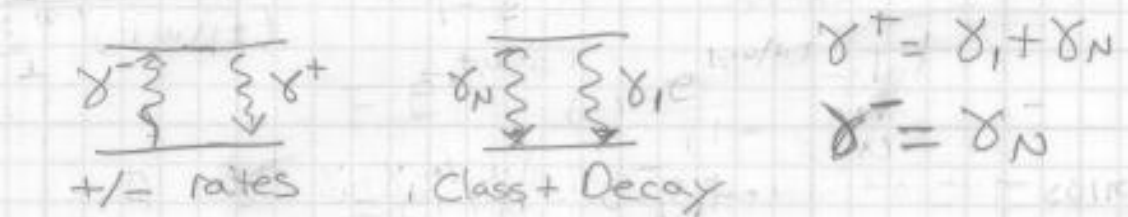

③ $\frac{S_I^{\text{qu}}(-\omega/2\pi)}{S_I^{\text{qu}}(+\omega/2\pi)} = e^{-\hbar\omega/kT}$ 2 transition rates give Boltz factor correctly

④ $S_I^+(\omega/2\pi) = S_I^{\text{qu}}(-\omega/2\pi) + S_I^{\text{qu}}(\omega/2\pi)$ Single-Sided Spectrum

(do math) $= 2\hbar\omega \coth(\hbar\omega/2kT) \operatorname{Re}\left(\frac{1}{\epsilon}\right)$

$\rightarrow 4kT \operatorname{Re}\left(\frac{1}{\epsilon}\right) \quad \hbar\omega \ll kT$

Johnson/Nyquist Noise of R

Measurement of Quantum Noise

Voltage state of CBJJ : HF noise mixed to LF

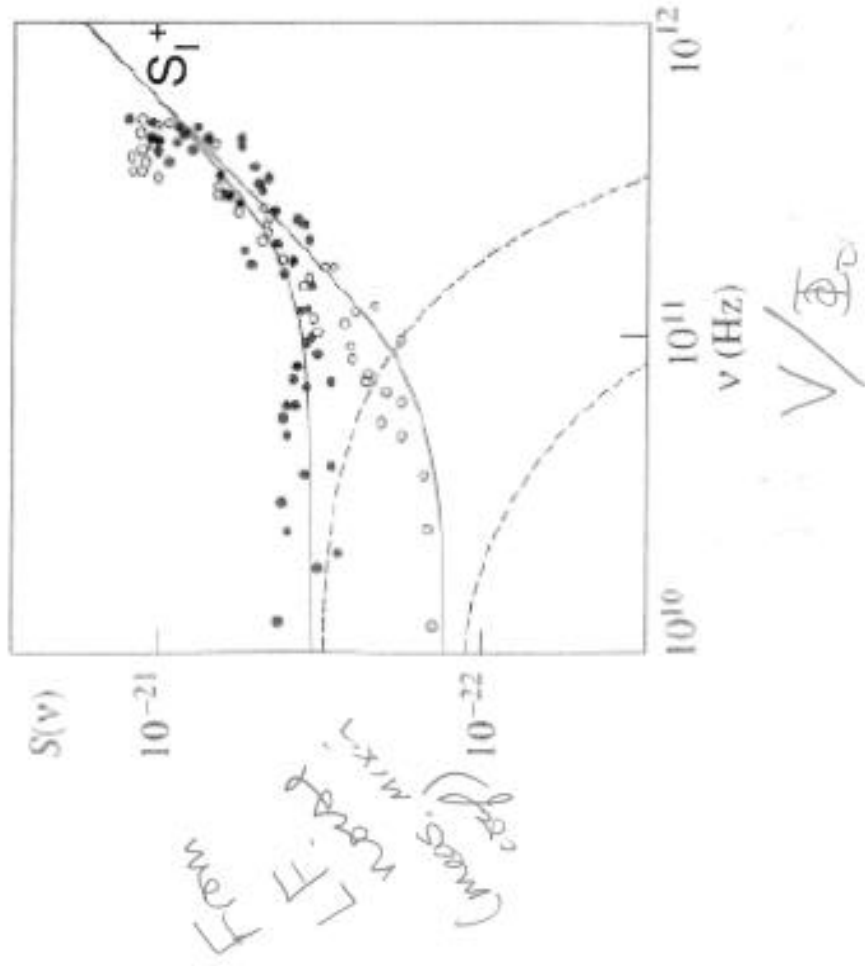


Fig. 1.2 Measured spectral density of noise current in the experiment of *Koch et al.* at 4.2 K (solid circles) and 1.6 K (hollow circles). The solid lines are the prediction of (1.2.5), while the dashed lines correspond to the Planck spectrum (1.2.3)

Like X, Y op's, Z op's need double-sided spectrum. To express as show previously (with 1-sided integral),

Use S_{\pm}^+ to integrate both \pm frags.

$$\langle \phi_N^z \rangle = \left(\frac{\partial \omega_{10}}{\partial I} \right)^2 \int_{-\infty}^{\infty} dF \omega_d(F) S_{\pm}^{\pm}(\omega_{10}/2\pi)$$

$$= \left(\frac{\partial \omega_{10}}{\partial I} \right)^2 \int_{-\infty}^{\infty} dF \omega_d(F) S_{\pm}^{\pm}(\omega_{10}/2\pi)$$

was Z.P. noise

included in this integral


↑
cotanh(\cdot) formula,
ZP noise included.

Using Noise


Decoherence = noise

→ How do I isolate my qubit from external world (which can drive noise into it?)

So far, shown HOW to calc. decoherence.

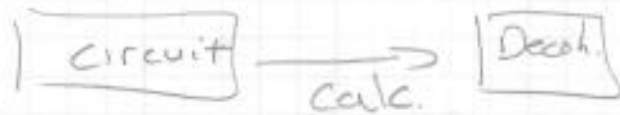


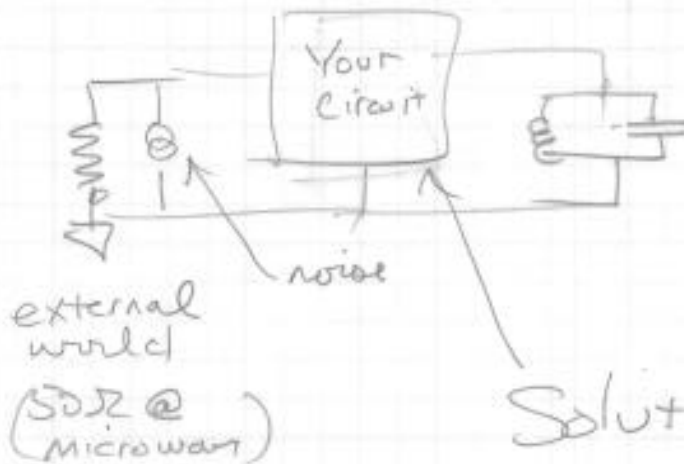→ Really interested in inverse problem, principles behind designing a good circuit



Solution: Build a circuit to reduce (atten.) current noise!

General Problem:


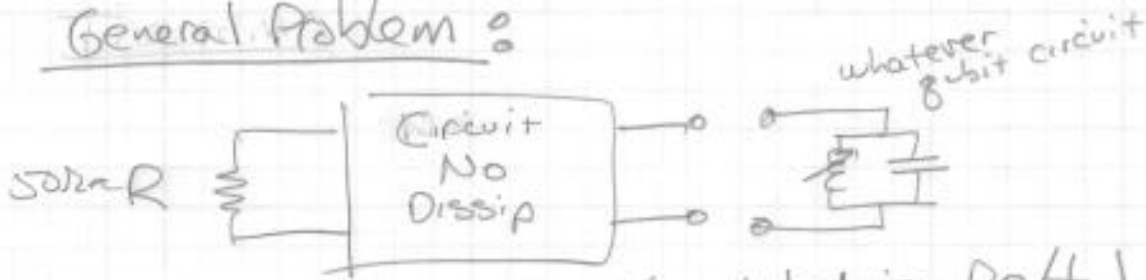


← what is $\text{Re}\left(\frac{1}{Z}\right)$

looking into loads

→ Tells us how external circuit loads/decoh qubit.

Solution:

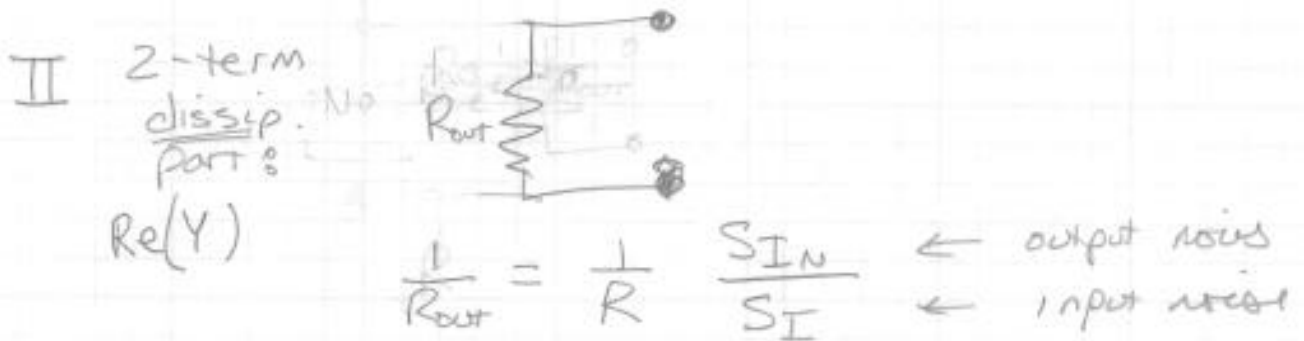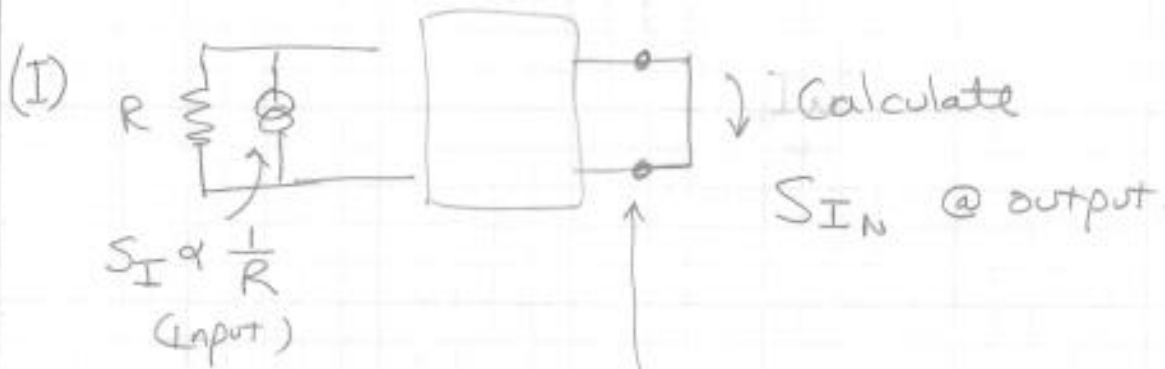


R_{out} is transformed up by $(\text{current})^2$ ratio!

(This is, in fact, a classical concept).

There are 3 example circuits that are used in qubit devices —

(It's the simplicity of this calcul. that is so useful — can calculate with normal Z methods used previously; intuition is the key!)


(1)

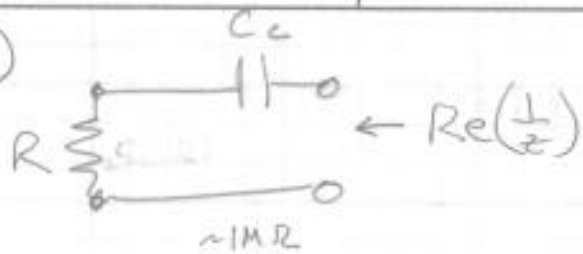

$$Z = R + \frac{1}{i\omega C_c}$$

$$\frac{1}{Z} = \frac{R - \frac{1}{i\omega C_c}}{R^2 + (\frac{1}{\omega C_c})^2}$$

normal calc.

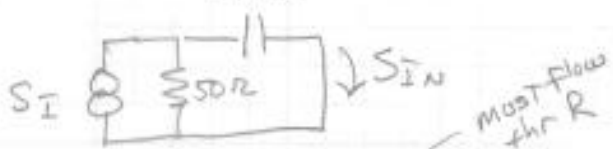


$$\frac{1}{R_{out}} = \text{Re}\left(\frac{1}{Z}\right) \approx R(\omega C_c)^2$$

$$\frac{1}{R_{out}} = R(\omega C_c)^2$$

$$S_{IN} = \frac{R^2}{(\frac{1}{\omega C_c})^2} S_{I,1}$$

$$\frac{1}{R_{out}} = \frac{1}{R} \frac{R^2}{(\frac{1}{\omega C_c})^2}$$

(2)

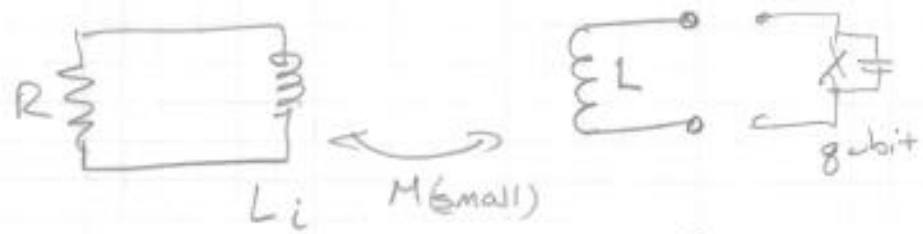

↳ assume $\omega L_i \ll R$



$$\Phi_2^2 = M^2 S_I$$


$$I_N = \frac{\Phi_2}{L}$$

$$S_{IN} = \left(\frac{M}{L}\right)^2 S_I$$



$$\frac{1}{R_{out}} = \left(\frac{M}{L}\right)^2 R \rightsquigarrow R_{out} \text{ transformed up by } \left(\frac{L}{M}\right)^2$$

$$50 \Omega \rightarrow (100)^2 50$$

$$\approx \frac{1}{2} M \Omega$$

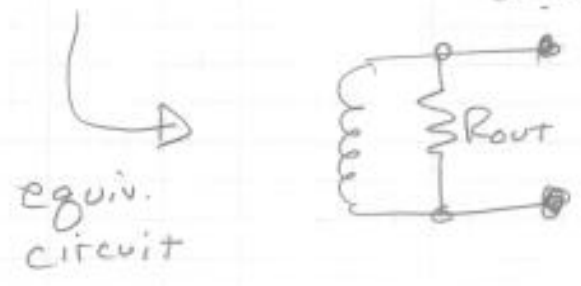


Variable Coupling SQUID Readout

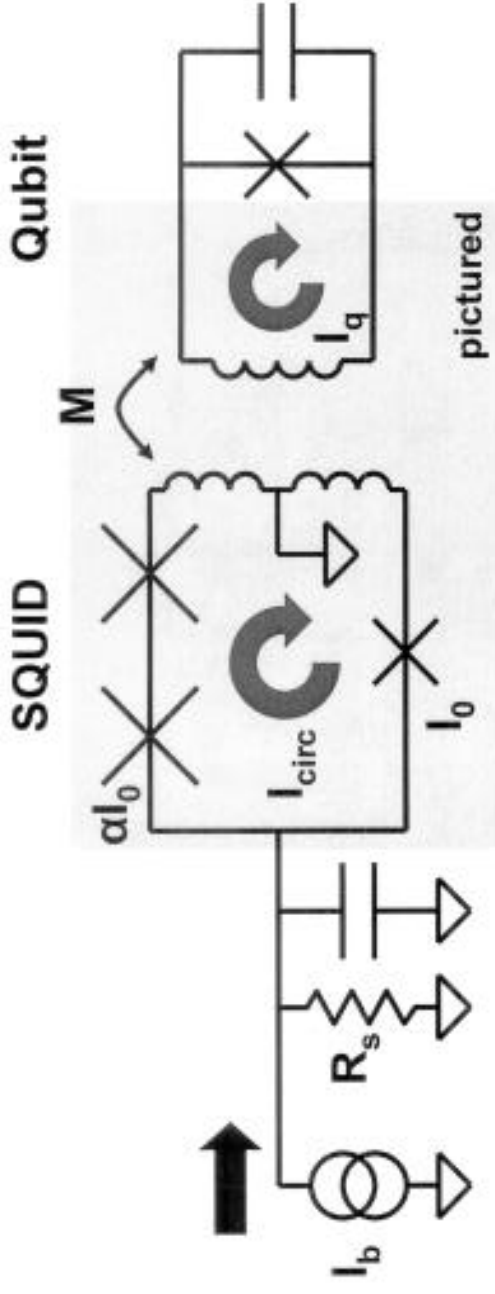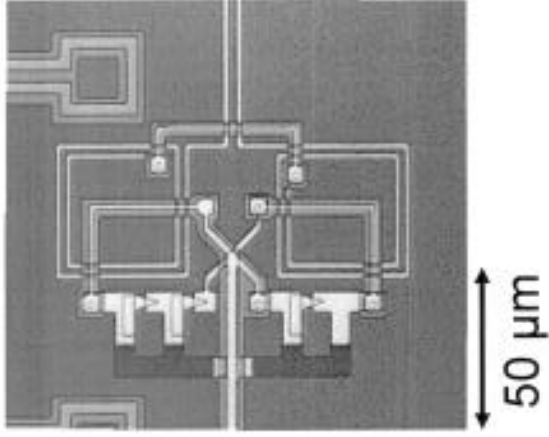

Squid is a variable transformer

Operation: squid balanced
 I_b chosen so I_{circ} is flat
 insensitive to flux

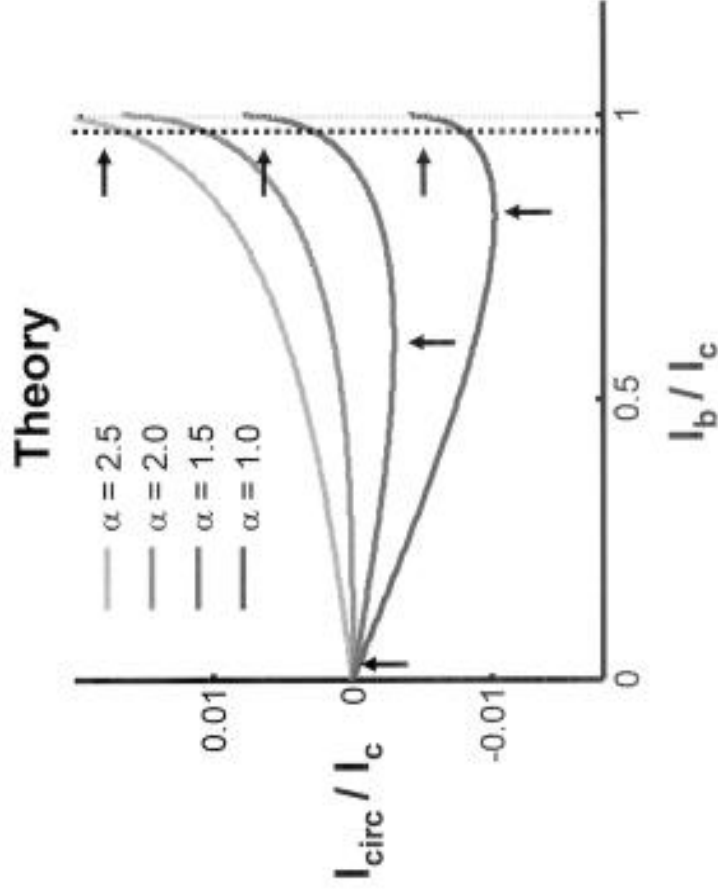
Measurement: squid unbalanced
 ramp $I_b \rightarrow I_c$, I_{circ} large
 sensitive to flux



Variable Impedance Transformer

Qubit dissipation from:

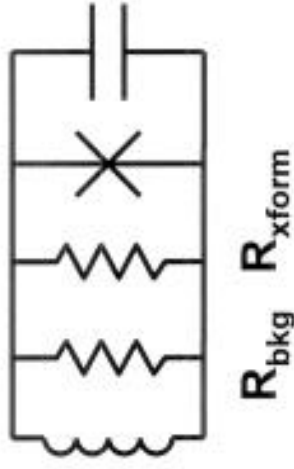- x-formed SQUID shunt R_s
- unknown "background" dissipation





$$R_{xform} = \frac{R_s}{(dI / dI_b)^2}$$

$$R_{tot} = R_{xform} \parallel R_{bkg}$$


$$T_1 = R_{tot} C$$

Best Fit to Data:

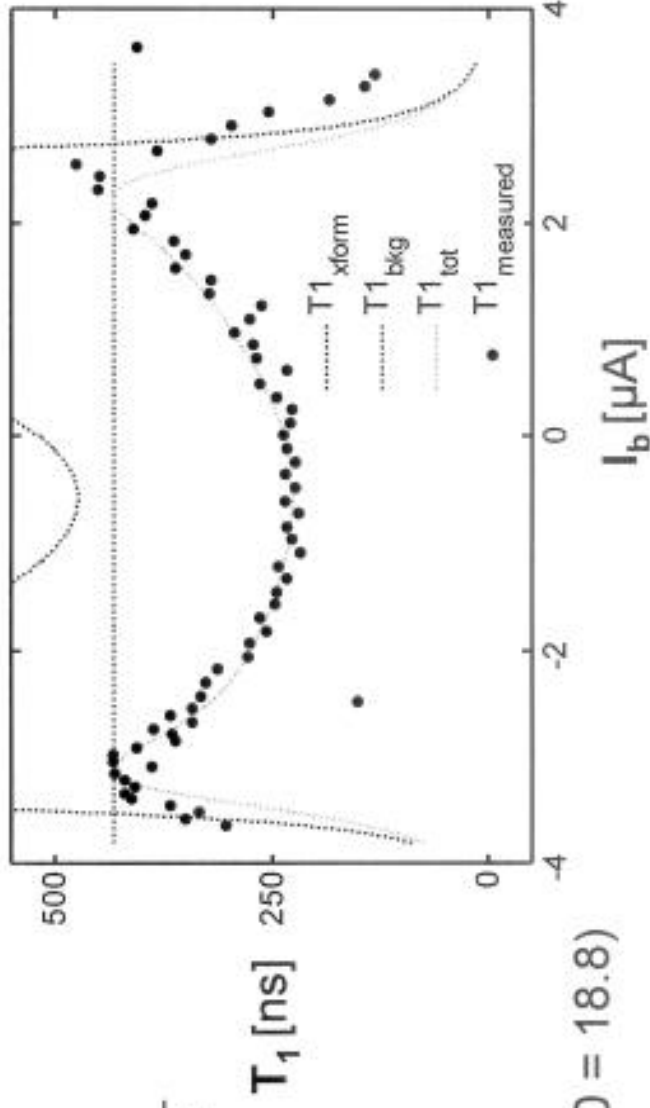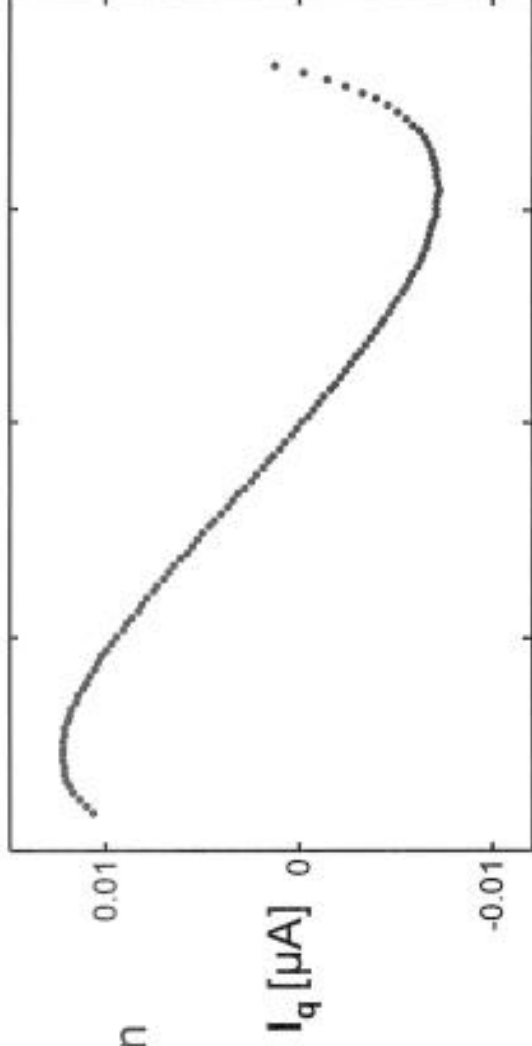- $T1_{bkg} = 433$ ns
- $R_s = 12.2 \Omega$ (expected $30 \parallel 50 = 18.8$)




(3) Tunable coupling (SQUID measmt.)

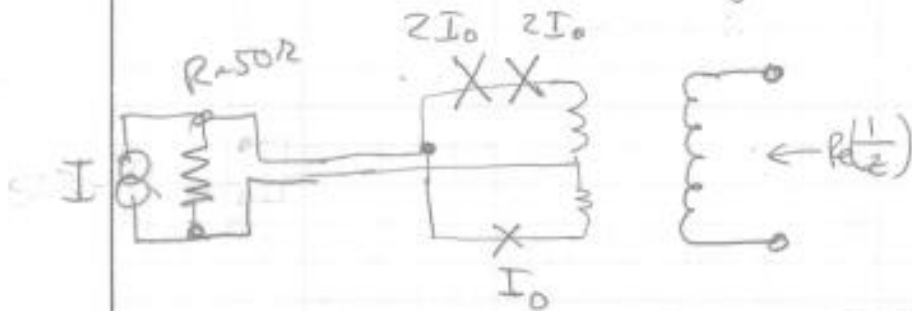

What is $Re(\frac{1}{zeta})$ w/ I ?

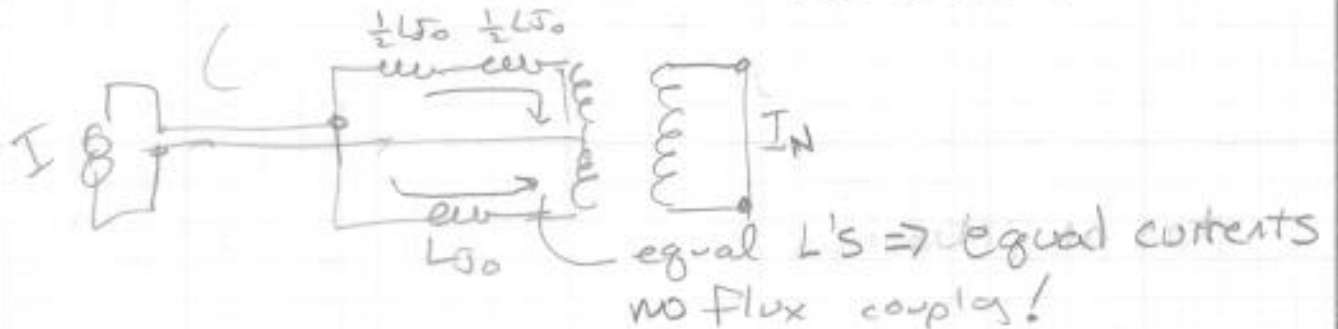At $I=0$ $L = \frac{\Phi_0}{2\pi I_0 \cos \delta}$; $L = L_{50}$ bottom
 $L = \frac{1}{2} L_{50}$ top



so $\frac{dI_N}{dI} = 0$; $Re(\frac{1}{zeta}) = 0$
 (∞ imped. transf.)

SQUID + Loop are decoupled

At large I ; current in lower branch reaches I_0 sooner, so $\cos \delta \rightarrow 0$ faster. More L_{50} reduces I relative to top, producing imbalance and thus Φ coupling.

$$\frac{1}{R_{out}} = \left(\frac{\partial I_N}{\partial I} \right)^2 \frac{1}{R}$$

↑ Calc. or measure.

- Show exp'l data.
- Go thr. all qubits + show transf structures

(1) Our Data for R transf.

(2) ϕ qubit; talk about 3 transformers

(3) q qubit

a) Eg μ waves.

b) Outside noise shunted by
Cap.

Large JJ. ($10 \times I_0$, smaller L)

b) Φ transf. to loop.



(4) Φ qubit


a) Φ coupling μ wave to SQUID loop.

b) I_b , C shunts out some I
Symmetry; I not couple to
flux (circ. current in loop).


(Φ bias changes + this coupling,
like ϕ qubit).

R Transformation : Phase Qubits

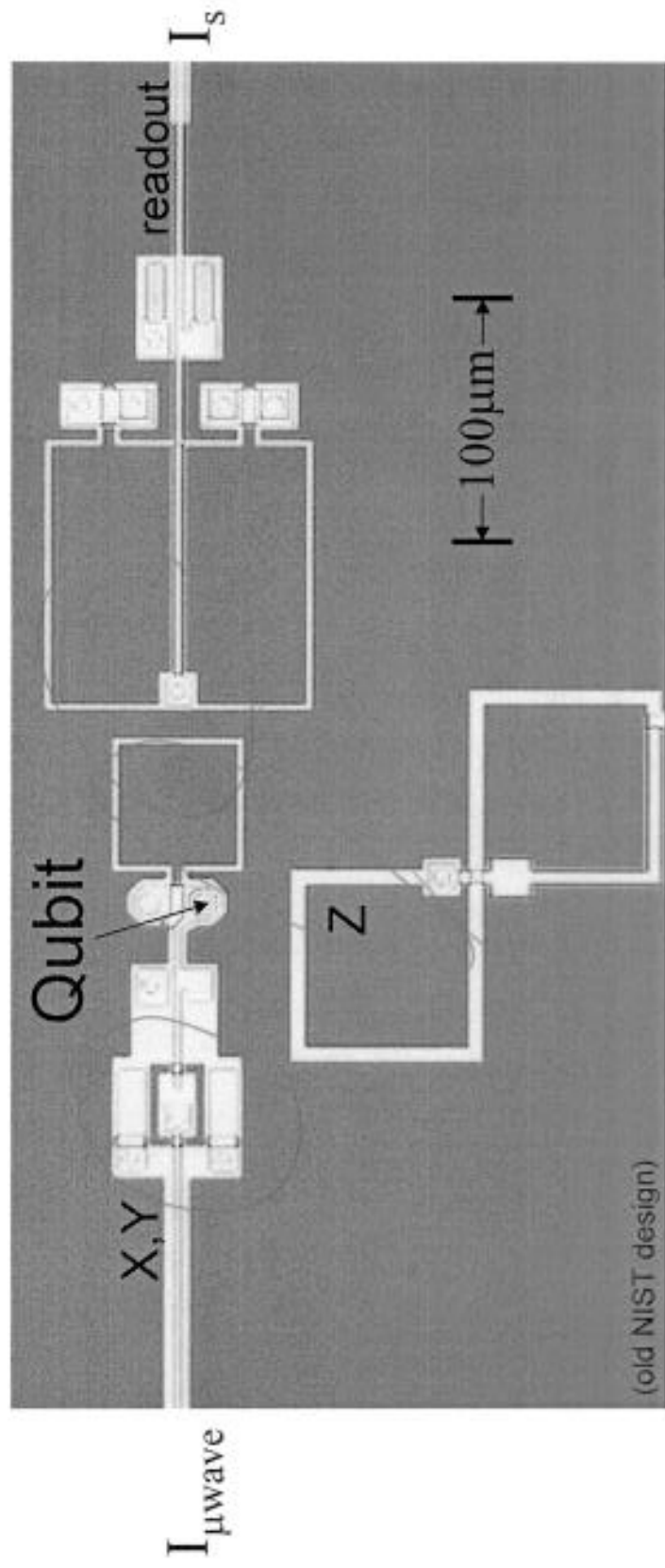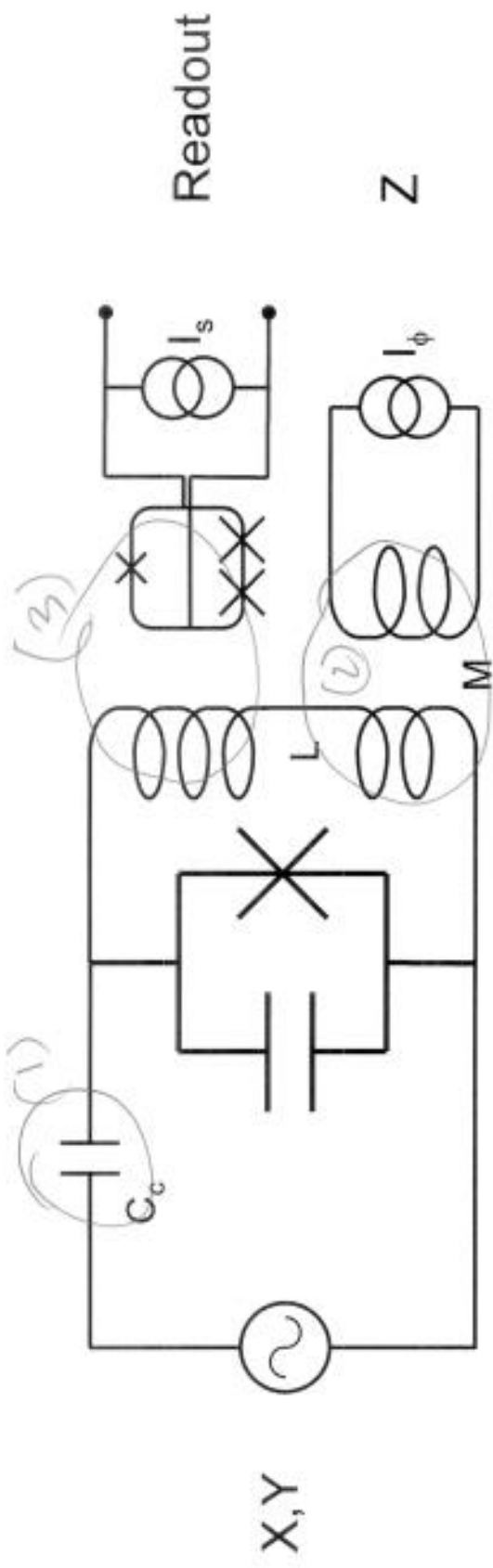

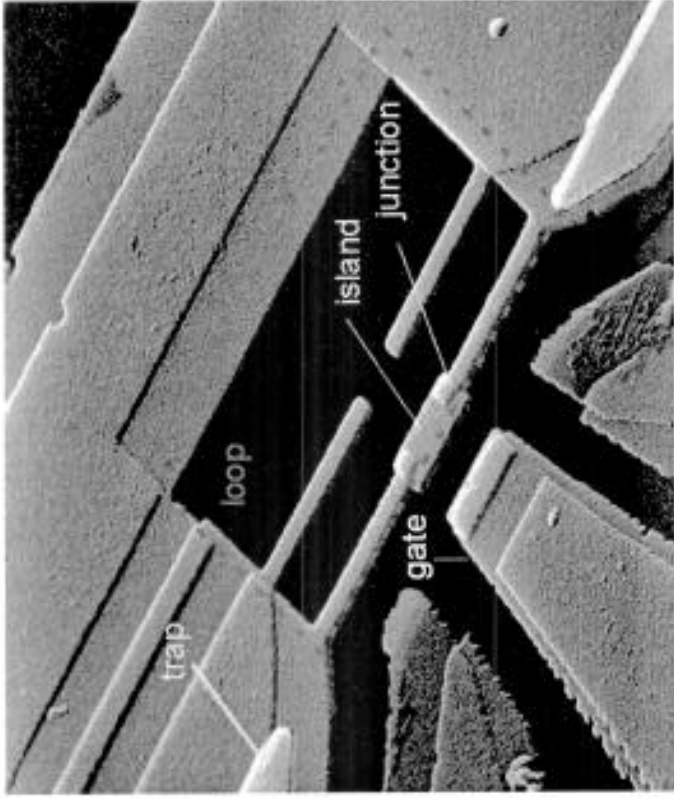

R Transformation : Charge Qubits

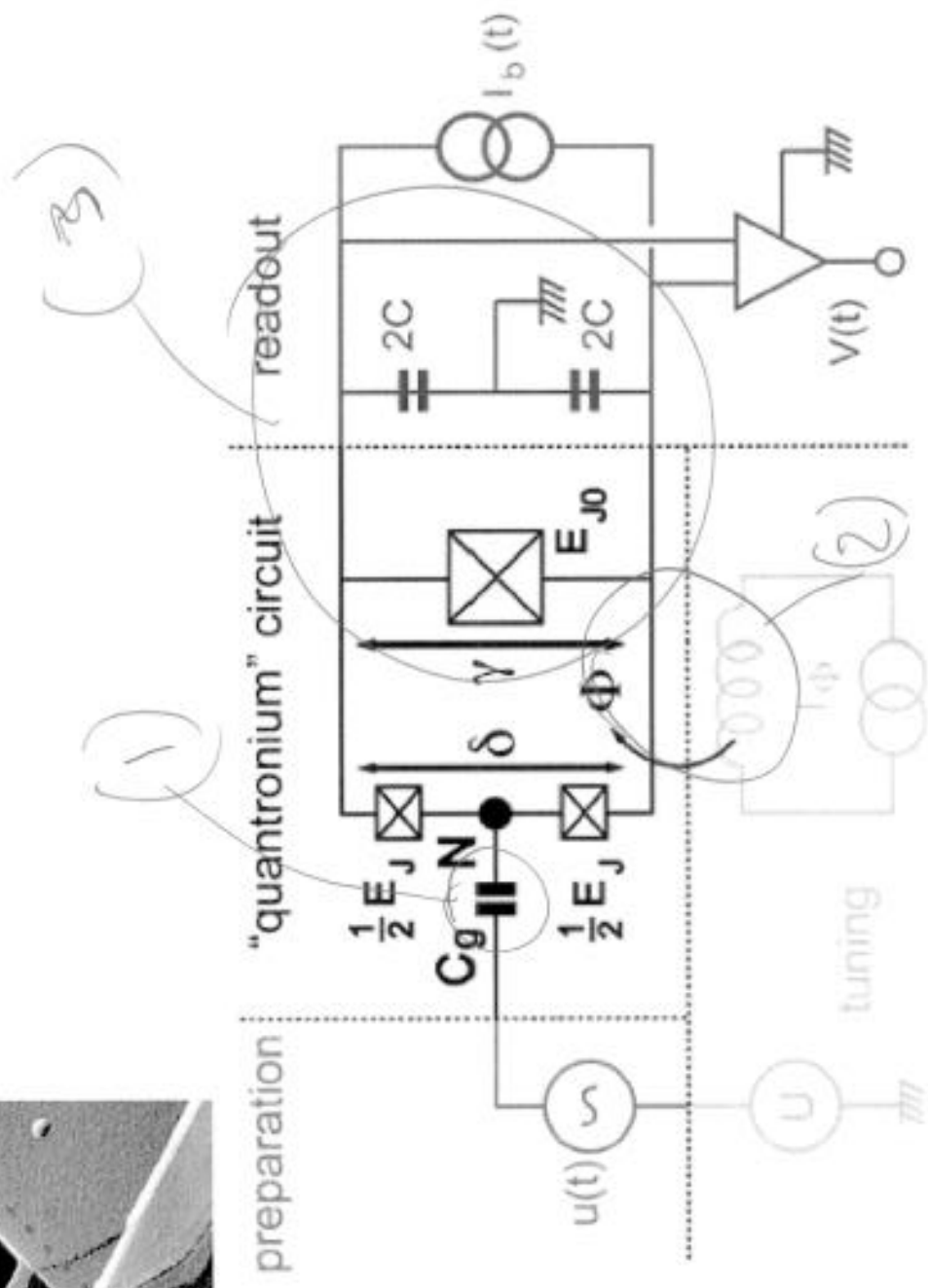

R Transformation: Flux Qubits

