

Demonstration 72.57 – LR circuit rise time (L/R)

$$i = \frac{\mathcal{E}}{R}(1 - e^{-Rt/L}), \text{ or}$$

$$i = \frac{\mathcal{E}}{R}(1 - e^{-t/\tau}), \text{ where } \tau = L/R$$

R , of course, changes as the lamp heats up. (At 120 V and maximum current the resistances are about 360Ω and 29Ω for the 40-watt and 500-watt lamps, respectively.) Still, we can estimate the L/R time constants for the lamps when they are cold. They are about $0.273 \text{ H}/28.5 \Omega = 9.6 \text{ ms}$, and $0.273 \text{ H}/1.6 \Omega = 170 \text{ ms}$, for the 40-watt and 500-watt lamps, respectively. These differ by a factor of about 18.

