

# Circuit Assembly Boot Camp

Version 2.0 Spring 2026 Professor Everett Lipman

Due **Thursday, May 14, at 11:59 P.M.**

Please note: There will be another lab due on Thursday, May 21, so **do not wait to get started!**

This boot camp will count as one lab. Each question or task has the point value shown in the corresponding box. You should have any available TA initial and score the box once you have completed the assigned question or task.

**1. Assemble a 555 Oscillator Circuit.** Begin where you left off in the Practical Electronics Boot Camp (available on the course web page). Turn off the potentiometer switch and your power supply. Cut and strip four 20 cm 22 AWG leads. Identify the front of the speaker from your boot camp project kit. The front has sound holes and a protected ring of adhesive around the rim. Solder the wires to the speaker terminals so that when the speaker faces you, the wires project away from you. The front of the speaker will eventually be attached to the inside wall of your project box.

Take one of the 500 kΩ potentiometers from your boot camp project kit and determine across which two terminals the resistance is minimized when the shaft is turned clockwise. This potentiometer will control frequency. We are choosing the terminals so that turning the shaft clockwise will raise the frequency, as one would expect intuitively. Keeping in mind that the wires must project away from you if the shaft is facing you, solder the two remaining leads to the terminals you selected.

*Have the TA check your speaker and 500 kΩ*

*potentiometer.* (4)

Read about the 555 timer integrated circuit (IC) in the handout on the course web page. Although you may not yet understand how the 555 works, you should be able to learn what it does.

Get a 7555 IC from the drawer in the lab. The 7555 is the CMOS version of the 555, and can be used in its place. Locate the 1 kΩ resistor and one of the 0.01 μF capacitors from your boot camp project kit, and the 500 kΩ potentiometer onto which you soldered the leads. Leave

the LED power indicator circuit in place on your breadboard.

Orient the 7555 IC so that you are looking down at the top of the package, and the indented notch or circle you see is to your left. The part numbers on the top of the package should now be upright. Carefully insert the IC into an unused section of your lower breadboard so that it straddles the center groove. If there is an IC insertion tool available in the lab, use it; this will help you avoid damaging the pins. Push the IC straight in so that the pins are properly seated in the sockets. With the notch to the left, pin 1 is at the lower left. Pin numbers increase going counterclockwise around the IC, so pin 4 is at the lower right, pin 5 is at the upper right, and pin 8 is at the upper left, above pin 1. See page 142 (1st edition: 153) in MkE if you are confused.

Using the multimeter, set the resistive part of your 5 kΩ potentiometer to about 50 Ω. Set the 500 kΩ potentiometer to about 300 kΩ. Neatly assemble on your breadboard the oscillator circuit shown in Fig. 1. Connect pin 3 of the IC to one of the leads from the resistive part of your 5 kΩ potentiometer. Connect the other 5 kΩ potentiometer lead to one of your speaker leads. Connect the remaining speaker lead to the positive rail.

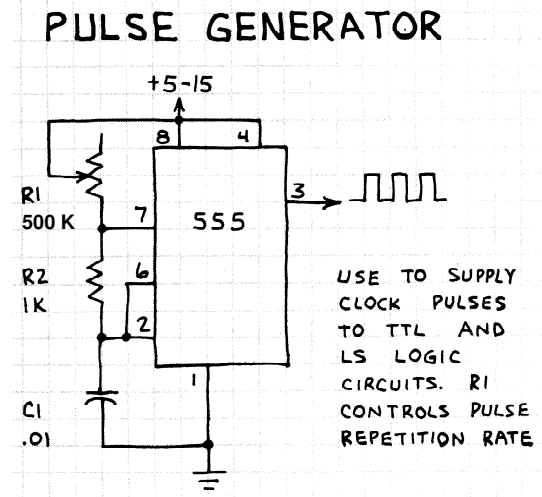


Figure 1: 555 oscillator circuit.



the power indicator circuit switch is between the “+5–15” V terminal in Fig. 2 and the supply, so that you can turn off the circuit with the switch. Avoid running components and wires over the IC when you assemble this circuit. Instead, route them to the side. This will make your life a lot easier when you transfer the circuit to the perfboard.

It is helpful to use the part of your breadboard with the same hole numbering as the perfboard in your parts kit. Then you will be able to transfer the circuit as-is for soldering. Avoid using the two columns on the far right and far left of the perfboard. Wires in these columns could interfere with the posts in the project box that support the perfboard.

Turn on the power supply and set it to +9 V. Check your connections, then turn on the circuit switch. Experiment with the two 500 k $\Omega$  potentiometers.

Demonstrate your circuit for the TA.

(5) \_\_\_\_\_

**4. Solder the 556 Sound Synthesizer Circuit.** Read pages 168–175 (1st ed: 137–144) in MKE. Locate and examine the perfboard and IC socket in your boot camp parts kit. We will use the IC socket when soldering the circuit together in order to avoid the risk of permanent heat damage to the IC.

Check the layout of your 556 circuit on the breadboard. If there are any improvements to be made, now is the time. Recheck the circuit after each change.

Transfer the power indicator and 556 sound synthesizer circuits from the breadboard to the perfboard. Solder one component at a time, and use the socket in place of the IC. Find the notch in the IC socket, and position it on your perfboard so that it will match the notch or circle on the 556 IC. Replace the power supply connections with your 9 V battery clip.

Use the “Helping Hand” holder to keep your hands free while you solder. You can temporarily hold components in place with tape if necessary. Avoid shorting adjacent pads when you solder.

When you are finished, check your connections. Then, check your connections. Fix any mistakes you find. Paying very careful attention to proper orientation and pin alignment, push the 556 IC into the socket. If one is available in the lab, use an IC insertion tool to do this. Check your connections and the IC orientation. Connect the battery to the clip and turn on the power.

Demonstrate your circuit for the TA.

(20) \_\_\_\_\_

In order for you to proceed, your soldered 556 sound synthesizer circuit, including the power indicator LED, must be completely functional.

Demonstrate for the TA that your circuit is functioning

flawlessly. (P/F) \_\_\_\_\_

**5. Install the 556 Sound Synthesizer in an enclosure.** You will now assemble the sound synthesizer circuit and the project box in your parts kit to make a complete device.

Examine the layout of the project box. Notice how the mounted components, battery, and circuit board have been placed in the box so that there is no contact between them when the lid is closed. The wires should be coiled so that when the box is opened, they will stretch without getting tangled. The exterior layout has been designed rationally, so that the power indicator is closest to the shaft that turns on the device. The two control potentiometer shafts have been placed using a symmetric arrangement that suggests their functions are different from that of the volume/power shaft. The shafts all have sufficient clearance to allow for installation of knobs. Notice which hardware is screwed onto the potentiometer shafts from outside the box, and pay attention to how the bent tabs protruding from the potentiometer cases prevent rotation.

**6. Install the 556 Sound Synthesizer in your Enclosure.** Once you understand the layout of the project box, install the components, circuit board, and battery. When closing your project box, make sure the lid is properly seated by sliding the tabs on the lid straight into the slots on the box. Tighten the screws until they are slightly snug. *Do not overtighten the screws!* It is easy to destroy the plastic underneath the screw heads. Test your project thoroughly and fix any problems before having it graded.

Your grade will be based on the quality of your project, as determined by the TAs using the guidelines below. Please present your finished project to a TA for grading.

*The exterior appearance of the project should be professional, with the controls, power indicator, and*

speaker properly placed. There should be no visible assembly errors. (10) \_\_\_\_\_

The device should turn on and off when the switch on the volume control potentiometer is flipped.

(3) \_\_\_\_\_

The power indicator LED should be mounted properly, and should function correctly.

(3) \_\_\_\_\_

The volume control potentiometer should be mounted properly, and should function correctly. The volume should increase when the shaft is turned clockwise.

(4) \_\_\_\_\_

The speaker should be mounted properly, and should function correctly. It should easily be heard.

(4) \_\_\_\_\_

The control knobs should be mounted properly, and both should affect the output sound in the expected manner. Turning either shaft clockwise should

increase frequency. (10) \_\_\_\_\_

Inside the box, the circuit board should be mounted securely on two posts. (4) \_\_\_\_\_

The battery should be held in place properly by the clip. (4) \_\_\_\_\_

There should be clearance for all components and wires when the box is open and closed.

(5) \_\_\_\_\_

The wiring inside the box should be correct, neat, easy to follow, and not prone to tangling. Opening the box should not cause any wiring problems. There should not be any excess bare wire that could cause

short circuits. (10) \_\_\_\_\_

## Parts List

Quantity	Item
2	500 k $\Omega$ linear taper potentiometer
1	5 k $\Omega$ audio taper potentiometer with switch
1	1 k $\Omega$ resistor
1	390 $\Omega$ resistor
1	8 $\Omega$ speaker
1	NE556 IC
1	14-pin IC socket
2	0.01 $\mu$ F (10 nF) capacitor
1	miniature perfboard
1	project box with hardware
1	9 V battery clip
1	5 mm LED
1	5 mm LED holder