

**Physics 127A — Practice Exam**

Spring 2026


Professor Everett Lipman

Thursday, June 11, 12:00–3:00 p.m.

Phelps 2524

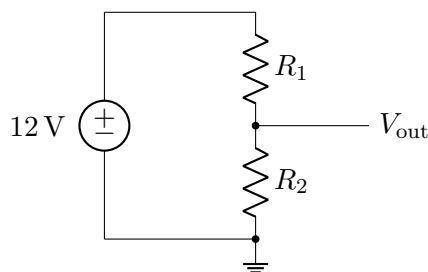**Problem 1. Resistive network, Thevenin equivalent, and power [10 pts]**


The circuit below is driven by an ideal 12 V source.  $R_1 = 1\text{ k}\Omega$  and  $R_2 = 2\text{ k}\Omega$ .




- With nothing connected at  $V_{\text{out}}$ , find  $V_{\text{out}}$ . [2]
- Find the Thevenin equivalent resistance seen looking back into the  $V_{text{out}}$  terminal (source replaced by its internal impedance). [2]
- A load  $R_L = 1\text{ k}\Omega$  is now connected from  $V_{\text{out}}$  to ground. Find the new value of  $V_{\text{out}}$ . [4]
- For the loaded circuit of part (c), find the power dissipated in  $R_1$ . [2]

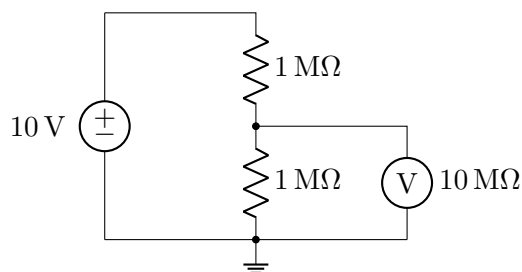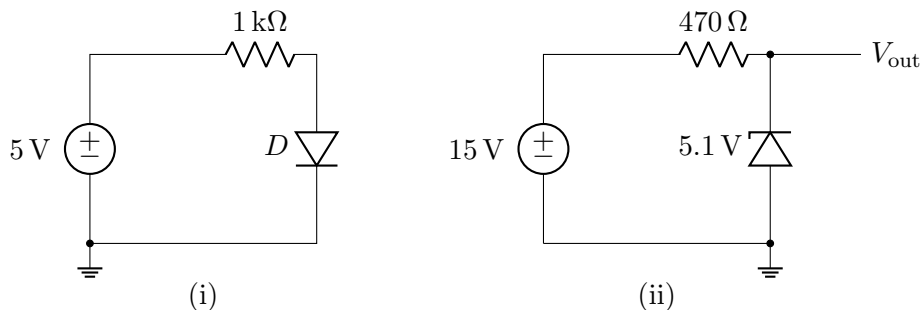**Problem 2. Non-ideal measuring instruments [10 pts]**

- A divider is built from two equal  $1\text{ M}\Omega$  resistors across a  $10\text{ V}$  source; the midpoint is the output. An analog voltmeter with input resistance  $10\text{ M}\Omega$  is connected from the midpoint to ground. What voltage does it read, and what is the percentage error relative to the unloaded midpoint voltage? [4]




- An ammeter with  $1\text{ }\Omega$  of internal resistance is placed in series with a  $100\text{ }\Omega$  resistor across a  $10\text{ V}$  source. What current does it read, and by what percentage does this differ from the true (meterless) current? [3]
- An oscilloscope input is modeled as  $1\text{ M}\Omega$  in parallel with  $20\text{ pF}$ . At what signal frequency does the magnitude of the capacitive reactance equal the  $1\text{ M}\Omega$  resistance? State the qualitative consequence for high-frequency measurements. [3]

**Problem 3. Diodes and a Zener regulator [10 pts]**

- In circuit (i), find the current through the diode. [2]
- In circuit (ii) with *no* load attached at  $V_{\text{out}}$ , find the current through the series resistor and the power dissipated in the Zener diode. [3]
- A load is now attached at  $V_{\text{out}}$  that draws 10 mA. Find the Zener current and state whether the output is still regulated. [2]
- What is the largest load current the circuit can supply before the output falls below 5.1 V? [3]

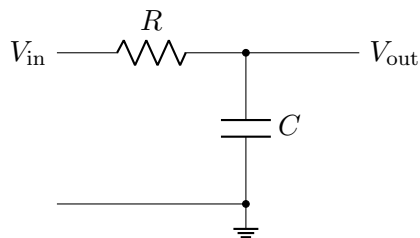**Problem 4. Reactive circuit: passive filter [10 pts]**


For the network below,  $R = 1 \text{ k}\Omega$  and  $C = 0.1 \text{ }\mu\text{F}$ .



- Is this a high-pass or low-pass filter? Find its  $-3 \text{ dB}$  (corner) frequency  $f_c$  in hertz. [3]
- Write the complex transfer function  $V_{\text{out}}/V_{\text{in}}$  and evaluate its magnitude in dB at  $f = f_c$ . [3]
- Find the gain in dB and the phase shift one decade above  $f_c$ , i.e. at  $f = 10f_c$ . [2]
- A sinusoid of amplitude 2 V at  $f = f_c$  is applied at  $V_{\text{in}}$ . Give the amplitude and phase of  $V_{\text{out}}$ . [2]

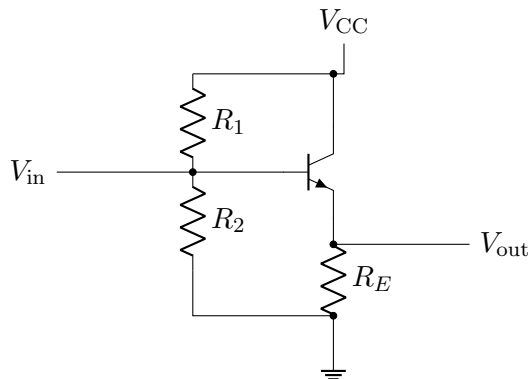**Problem 5. BJT emitter follower [10 pts]**


$V_{\text{CC}} = 15 \text{ V}$ ,  $R_1 = R_2 = 100 \text{ k}\Omega$ ,  $R_E = 6.8 \text{ k}\Omega$ . The transistor is an NPN with  $\beta = 100$ .



- Find the quiescent base voltage  $V_B$ , emitter voltage  $V_E$ , and collector current  $I_C$ . [3]
- Find the small-signal input impedance looking into the base, and then the input impedance of the whole stage (including the bias resistors). [3]
- The stage is driven from a source of resistance  $R_s = 1\text{ k}\Omega$ . Estimate the output impedance at the emitter. [2]
- Find the small-signal voltage gain  $V_{\text{out}}/V_{\text{in}}$ . [2]


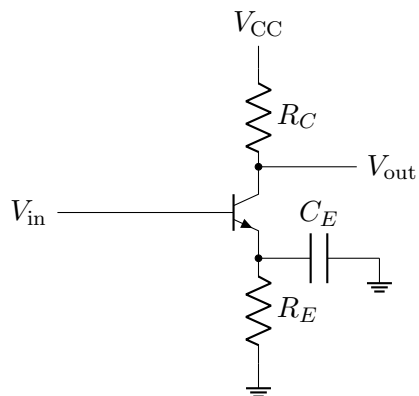
**Problem 6. BJT common-emitter amplifier [10 pts]**

$V_{CC} = 15\text{ V}$ ,  $R_C = 5\text{ k}\Omega$ ,  $R_E = 2\text{ k}\Omega$ . The bias network (not all shown) holds the base at  $V_B = 2.6\text{ V}$ . For AC signals the emitter is connected to ground through a large bypass capacitor.



- Find the quiescent collector current  $I_C$  and collector voltage  $V_C$ . Confirm the transistor is in the active region. [3]
- With the emitter fully bypassed, find the small-signal voltage gain. Use  $r_e = 25\text{ }\Omega/I_C(\text{mA})$ . [3]
- Express the magnitude of the gain from part (b) in decibels. [2]
- Now suppose a  $100\text{ }\Omega$  resistor is left *unbypassed* in series with the emitter. Find the new voltage gain. [2]

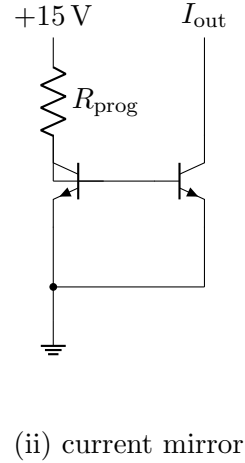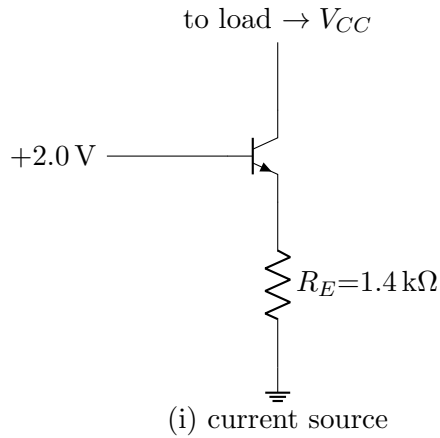
**Problem 7. BJT current source and current mirror [10 pts]**



- Starting from the Ebers–Moll relation, derive the intrinsic emitter resistance  $r_e = V_T/I_C$  and evaluate it at  $I_C = 1 \text{ mA}$ ,  $20^\circ\text{C}$ . [3]
- In current source (i) the base is held at  $2.0 \text{ V}$ . Find the output current delivered to the load. [2]
- For a  $15 \text{ V}$  supply, over what range of load voltage does the source in (i) maintain a nearly constant current? (Take the saturation limit as  $V_{CE} \geq 0.2 \text{ V}$ .) [2]
- In mirror (ii), choose  $R_{\text{prog}}$  so that  $I_{\text{out}} = 1 \text{ mA}$ , and explain in one or two sentences why the output current mirrors the programming current. [3]

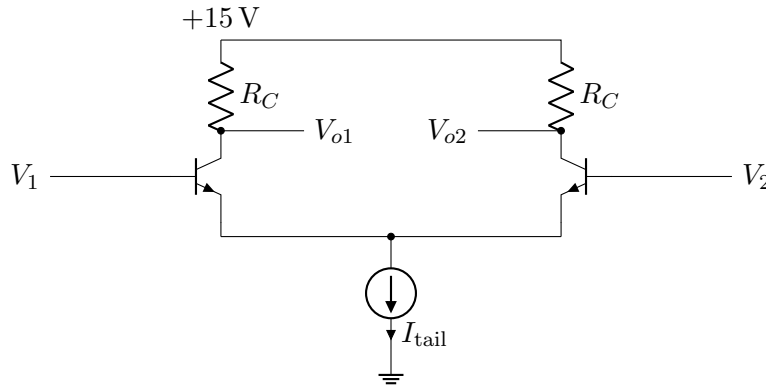**Problem 8. BJT differential amplifier [10 pts]**

Two matched NPN transistors share a tail current source  $I_{\text{tail}} = 2 \text{ mA}$ . Each collector resistor is  $R_C = 7.5 \text{ k}\Omega$  to a  $15 \text{ V}$  supply.  $\beta = 100$ .




- Find the quiescent collector current in each transistor and the DC voltage at each collector. [2]
- Find the differential gain to a single collector,  $v_{o1}/(V_1 - V_2)$ , and the collector-to-collector differential gain. [3]
- The tail current source has an output resistance  $R_{\text{tail}} = 500 \text{ k}\Omega$ . Find the single-ended common-mode gain and the common-mode rejection ratio (CMRR) in dB. [3]

- (d) Find the small-signal input impedance at one base and the output impedance at one collector. [2]

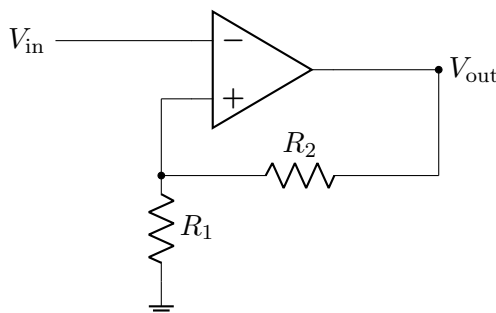**Problem 9. Schmitt trigger [10 pts]**


The comparator below uses positive feedback. The op amp output saturates at  $\pm 12\text{ V}$ . The resistor  $R_1 = 10\text{ k}\Omega$  runs from the non-inverting input to ground and  $R_2 = 20\text{ k}\Omega$  runs from the output back to the non-inverting input; the signal  $V_{\text{in}}$  drives the inverting input directly.



- (a) Explain why returning the feedback to the non-inverting input produces *positive* feedback, and state the input impedance this circuit presents to the source driving  $V_{\text{in}}$ , with a one-line justification. [3]
- (b) Find the voltage at the non-inverting input in each of the two output states, and hence the two input threshold voltages at which the output switches. [3]
- (c) Give the width of the hysteresis. [2]
- (d) Keeping  $R_1 = 10\text{ k}\Omega$ , choose a new value of  $R_2$  that would halve the hysteresis width. [2]

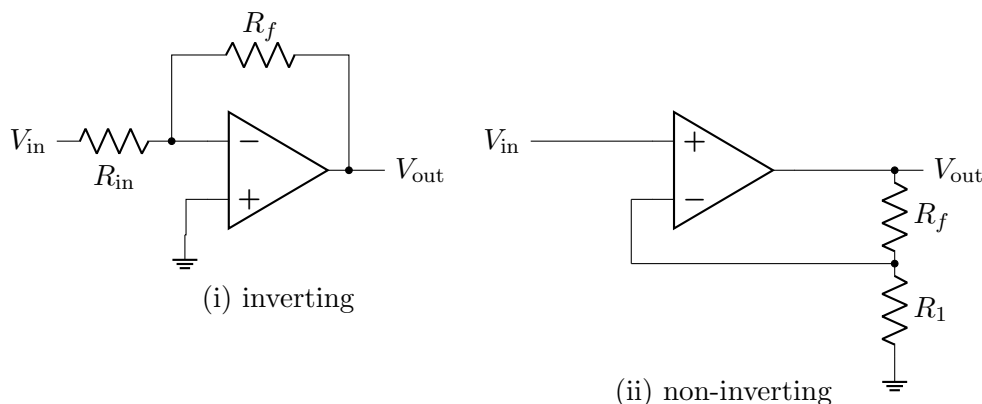**Problem 10. Operational amplifiers [10 pts]**

Assume ideal op amps unless stated otherwise.



- (a) State the two standard design approximations (“golden rules”) for an op amp operating with negative feedback. [2]
- (b) In the inverting amplifier (i),  $R_{\text{in}} = 10\text{ k}\Omega$  and  $R_f = 100\text{ k}\Omega$ . Find the voltage gain and the input impedance seen by the source. [2]

- (c) In the non-inverting amplifier (ii) with the same two resistor values ( $R_1 = 10\text{ k}\Omega$ ,  $R_f = 100\text{ k}\Omega$ ), find the voltage gain. How does its input impedance compare with that of (i)? [2]
- (d) Replace  $R_f$  in the inverting circuit with a capacitor  $C_f = 0.01\text{ }\mu\text{F}$  to make an integrator. Write  $V_{\text{out}}(t)$  in terms of  $V_{\text{in}}(t)$ , and find the frequency at which the magnitude of the gain equals unity. [2]
- (e) The op amp has a slew rate of  $1\text{ V}/\mu\text{s}$ . What is the highest frequency at which it can produce an undistorted sine wave of  $10\text{ V}$  amplitude at the output? [2]

**Constants and relations.**

$V_T \approx 25\text{ mV}$  at  $20^\circ\text{C}$ . Ebers–Moll:  $I_C = I_S(e^{V_{\text{BE}}/V_T} - 1)$ ,  $I_S \approx 10^{-13}\text{ A}$ .

Intrinsic emitter resistance:  $r_e \approx \frac{25\text{ }\Omega}{I_C(\text{in mA})}$ . Impedances:  $Z_C = \frac{1}{i\omega C}$ ,  $Z_L = i\omega L$ .

*Good luck.*