
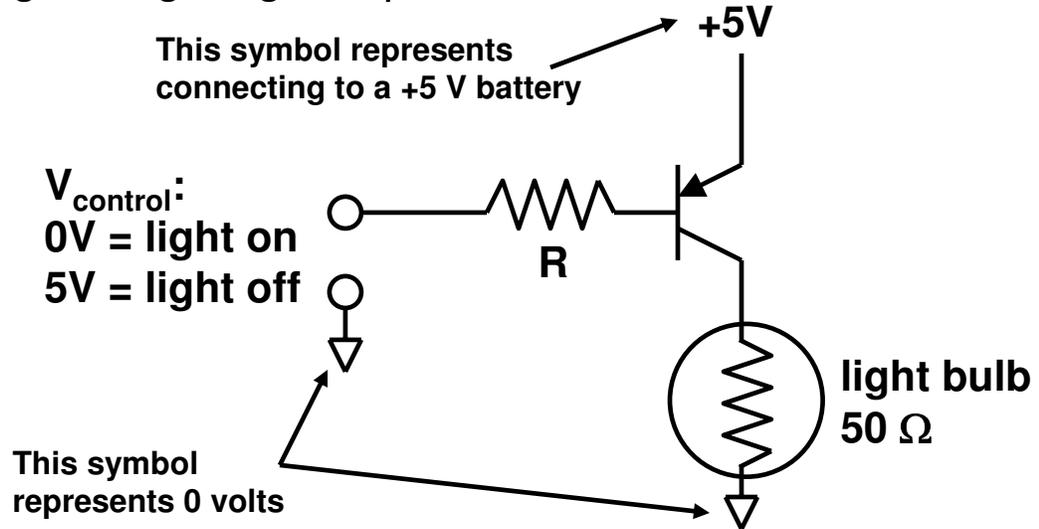


HW5, PHYSICS 127A

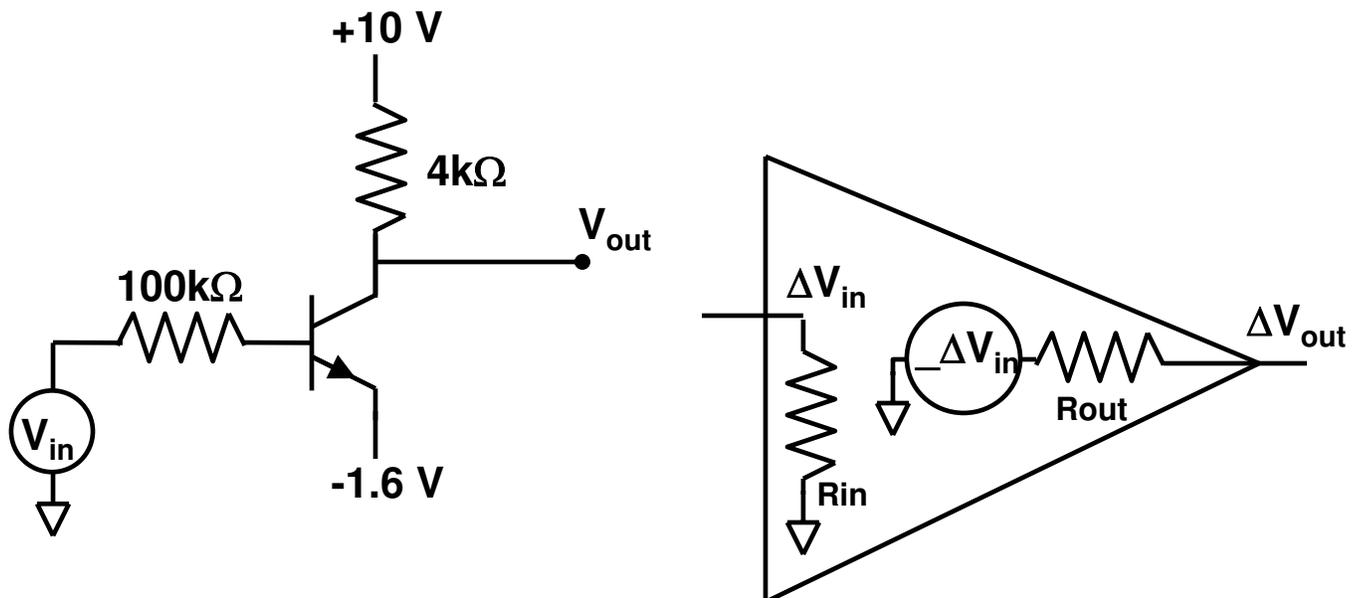
1. The following circuit is a lightbulb driver using a PNP transistor. Calculate R needed to drive the light bulb assuming $\beta = 100$. Don't forget the engineering margin for β .



2. (a) For the following circuit, plot as a function of V_{in} (from -2 to +3 volts) the base current, collector current, and V_{out} . (b) Compute the small-signal gain, input resistance, and output resistance for the equivalent amplifier model.



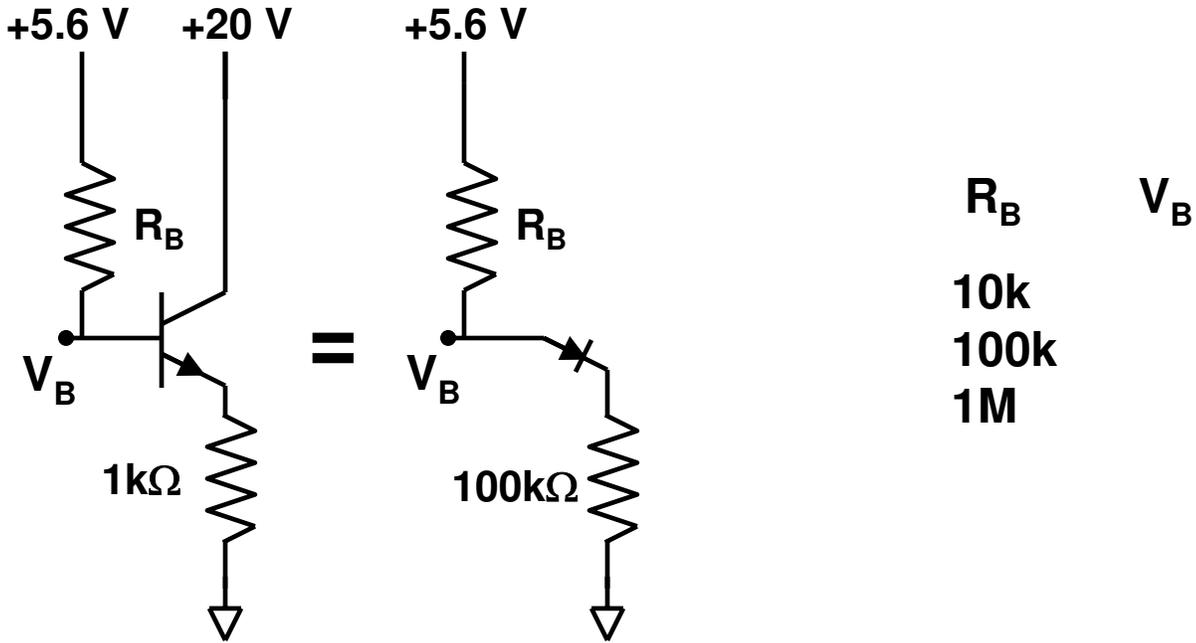3. (a) Assuming a transistor $\beta = 100$, show that the following two circuits are equivalent. (b) Compute the transistor base voltage for the values given in the table.



4. H.H. problem 2.2

5. H.H. problem 2.3

6. H.H. problem 2.4