

Name: \_\_\_\_\_ Perm #: \_\_\_\_\_ TA: \_\_\_\_\_

## **HW9, PHYSICS 127A**

- 1) Bad circuits D, F, and G; page 258.**
  
- 2) Design an amplifier with gain = -100 that has a “low pass” filter rolloff beginning at a frequency of 1 kHz.**

**Continued on next page...**

## HW9, PHYSICS 127A (CONTINUED)

Problems are embedded in text of Horowitz and Hill textbook.

- 3) HH 4.10 (Schmitt trigger).
- 4) Bad circuits I, K, M, and L on pages 259 & 260.
- 5) Sketch the gain versus frequency for the following two OpAmp amplifiers:

