

(44 points) HW #8 solutions  
Physics 23, Fall 06

(6 points)

**E31-8**  $(5.0 \text{ A})R_1 = \Delta V$ .  $(4.0 \text{ A})(R_1 + 2.0 \Omega) = \Delta V$ . Combining,  $5R_1 = 4R_1 + 8.0 \Omega$ , or  $R_1 = 8.0 \Omega$ .

**E31-22** Combining  $n$  identical resistors in series results in an equivalent resistance of  $r_{\text{eq}} = nR$ . Combining  $n$  identical resistors in parallel results in an equivalent resistance of  $r_{\text{eq}} = R/n$ . If the resistors are arranged in a square array consisting of  $n$  parallel branches of  $n$  series resistors, then the effective resistance is  $R$ . Each will dissipate a power  $P$ , together they will dissipate  $n^2 P$ .  
So we want nine resistors, since four would be too small.

**E31-38**  $r = \rho L / A = (3.5 \times 10^{-5} \Omega \cdot \text{m})(1.96 \times 10^{-2} \text{ m}) / \pi (5.12 \times 10^{-3} \text{ m})^2 = 8.33 \times 10^{-3} \Omega$ .  
(a)  $i = \sqrt{P/r} = \sqrt{(1.55 \text{ W}) / (8.33 \times 10^{-3} \Omega)} = 13.6 \text{ A}$ , so (4 points)

$j = i/A = (13.6 \text{ A}) / \pi (5.12 \times 10^{-3} \text{ m})^2 = 1.66 \times 10^5 \text{ A/m}^2$ .

(b)  $\Delta V = \sqrt{Pr} = \sqrt{(1.55 \text{ W})(8.33 \times 10^{-3} \Omega)} = 0.114 \text{ V}$ . (2 points)

**E31-44** (a)  $\Delta V = \mathcal{E}(1 - e^{-t/\tau_C})$ , so (2 points)

$\tau_C = -(1.28 \times 10^{-6} \text{ s}) / \ln(1 - 5.00 \text{ V} / 13.0 \text{ V}) = 2.64 \times 10^{-6} \text{ s}$

(b)  $C = \tau_C / R = (2.64 \times 10^{-6} \text{ s}) / (15.2 \times 10^3 \Omega) = 1.73 \times 10^{-10} \text{ F}$  (2 points)

**E31-45** (a)  $\Delta V = \mathcal{E}e^{-t/\tau_C}$ , so

$\tau_C = -(10.0 \text{ s}) / \ln(1.06 \text{ V} / 100 \text{ V}) = 2.20 \text{ s}$

(b)  $\Delta V = (100 \text{ V})e^{-17 \text{ s} / 2.20 \text{ s}} = 4.4 \times 10^{-2} \text{ V}$ .

**E31-46**  $\Delta V = \mathcal{E}e^{-t/\tau_C}$  and  $\tau_C = RC$ , so (6 points)

$$R = -\frac{t}{C \ln(\Delta V / \Delta V_0)} = -\frac{t}{(220 \times 10^{-9} \text{ F}) \ln(0.8 \text{ V} / 5 \text{ V})} = \frac{t}{4.03 \times 10^{-7} \text{ F}}$$

If  $t$  is between  $10.0 \mu\text{s}$  and  $6.0 \text{ ms}$ , then  $R$  is between

$R = (10 \times 10^{-6} \text{ s}) / (4.03 \times 10^{-7} \text{ F}) = 24.8 \Omega$ ,

and

$R = (6 \times 10^{-3} \text{ s}) / (4.03 \times 10^{-7} \text{ F}) = 14.9 \times 10^3 \Omega$ .

**P31-2** Traversing the circuit we have (6 points)

$\mathcal{E} - ir_1 + \mathcal{E} - ir_2 - iR = 0$ ,

so  $i = 2\mathcal{E} / (r_1 + r_2 + R)$ . The potential difference across the first battery is then

$$\Delta V_1 = \mathcal{E} - ir_1 = \mathcal{E} \left( 1 - \frac{2r_1}{r_1 + r_2 + R} \right) = \mathcal{E} \frac{r_2 - r_1 + R}{r_1 + r_2 + R}$$

This quantity will only vanish if  $r_2 - r_1 + R = 0$ , or  $r_1 = R + r_2$ . Since  $r_1 > r_2$  this is actually possible;  $R = r_1 - r_2$ .

**P31-10** We can assume that  $R$  "contains" all of the resistance of the resistor, the battery and the ammeter, then

$$R = (1.50 \text{ V}) / (1.0 \text{ mA}) = 1500 \Omega.$$

For each of the following parts we apply  $R + r = \Delta V / i$ , so

(a)  $r = (1.5 \text{ V}) / (0.1 \text{ mA}) - (1500 \Omega) = 1.35 \times 10^4 \Omega,$

(b)  $r = (1.5 \text{ V}) / (0.5 \text{ mA}) - (1500 \Omega) = 1.5 \times 10^3 \Omega,$

(c)  $r = (1.5 \text{ V}) / (0.9 \text{ mA}) - (1500 \Omega) = 167 \Omega.$

(d)  $R = (1500 \Omega) - (18.5 \Omega) = 1482 \Omega$

(8 points)

**P31-12**  $\Delta V_1 + \Delta V_2 = \Delta V_S + \Delta V_X$ ; if  $V_a = V_b$ , then  $\Delta V_1 = \Delta V_S$ . Using the first expression,

$$i_a(R_1 + R_2) = i_b(R_S + R_X),$$

using the second,

$$i_a R_1 = i_b R_2.$$

Dividing the first by the second,

$$1 + R_2/R_1 = 1 + R_X/R_S,$$

or  $R_X = R_S(R_2/R_1).$

(8 points)